

DL2WB 630 m TX antenna (ca. -38 dBi "gain" * at 476 kHz)

2017-05-05



loop circumference: ca. 16 m
 material: insulated, braided copper (e.g. old rotator control cable)
 wire cross-section: $13 \times 0.5 \text{ mm}^2 = 6.5 \text{ mm}^2$
 transformer winding ratio: coax-side : loop-side = 13:1



adjust transformer for R close to 50 Ohm:

$R < 50 \text{ Ohm}$:
increase number of windings on coax side

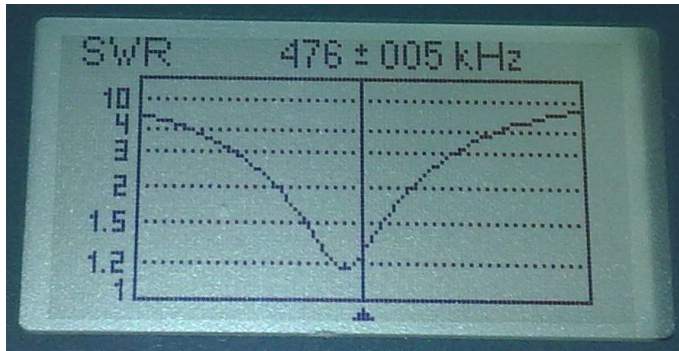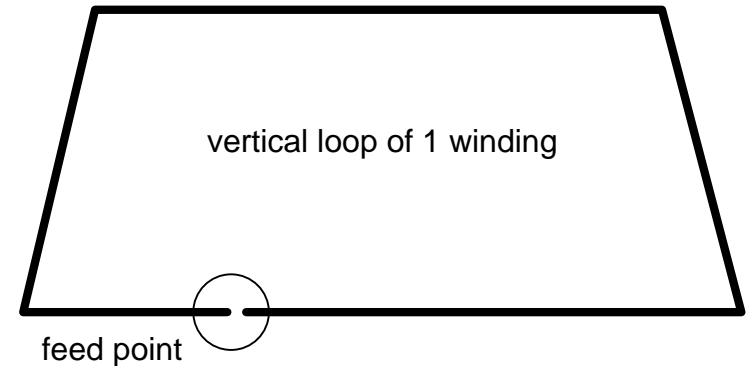
$R > 50 \text{ Ohm}$:
decrease number of windings on coax side



tune the capacitor to f_{target} :

$f_{\text{dip}} > f_{\text{target}}$:
increase capacitance

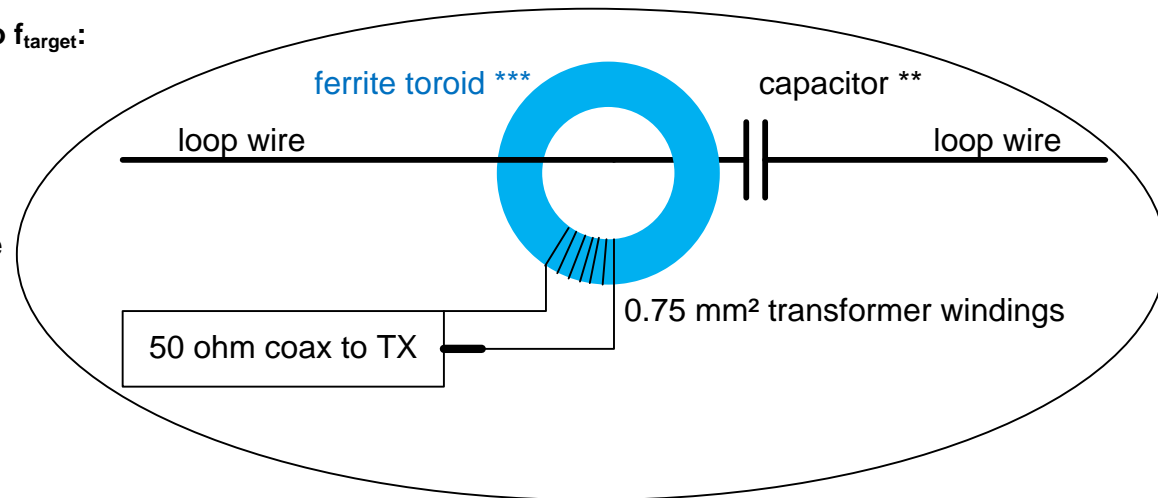$f_{\text{dip}} < f_{\text{target}}$:
decrease capacitance



* Magnetic loop calculator by DG0KW
<http://www.dl0hst.de/magnetlooprechner.htm>

** WIMA FKP 1 Polypropylene (PP) capacitors
 ca. 5 nF: 10 x 470 pF || + 1 x 100 pF || + (several 100 pF in series) ||
www.wima.com/EN/WIMA_FKP_1.pdf

*** N30 ferrite toroid TDK B64290L0048X830 (2 x || for 30 W TX power)
https://product.tdk.com/info/en/documents/data_sheet/R3400x2050x1250.pdf