

DX University: Smith Charts

2010 August 9

Sponsored by the South Florida




Kai Siwiak, ke4pt@amsat.org

Ed Callaway, n4ii@arrl.org


The Complete Smith Chart

Black Magic Design

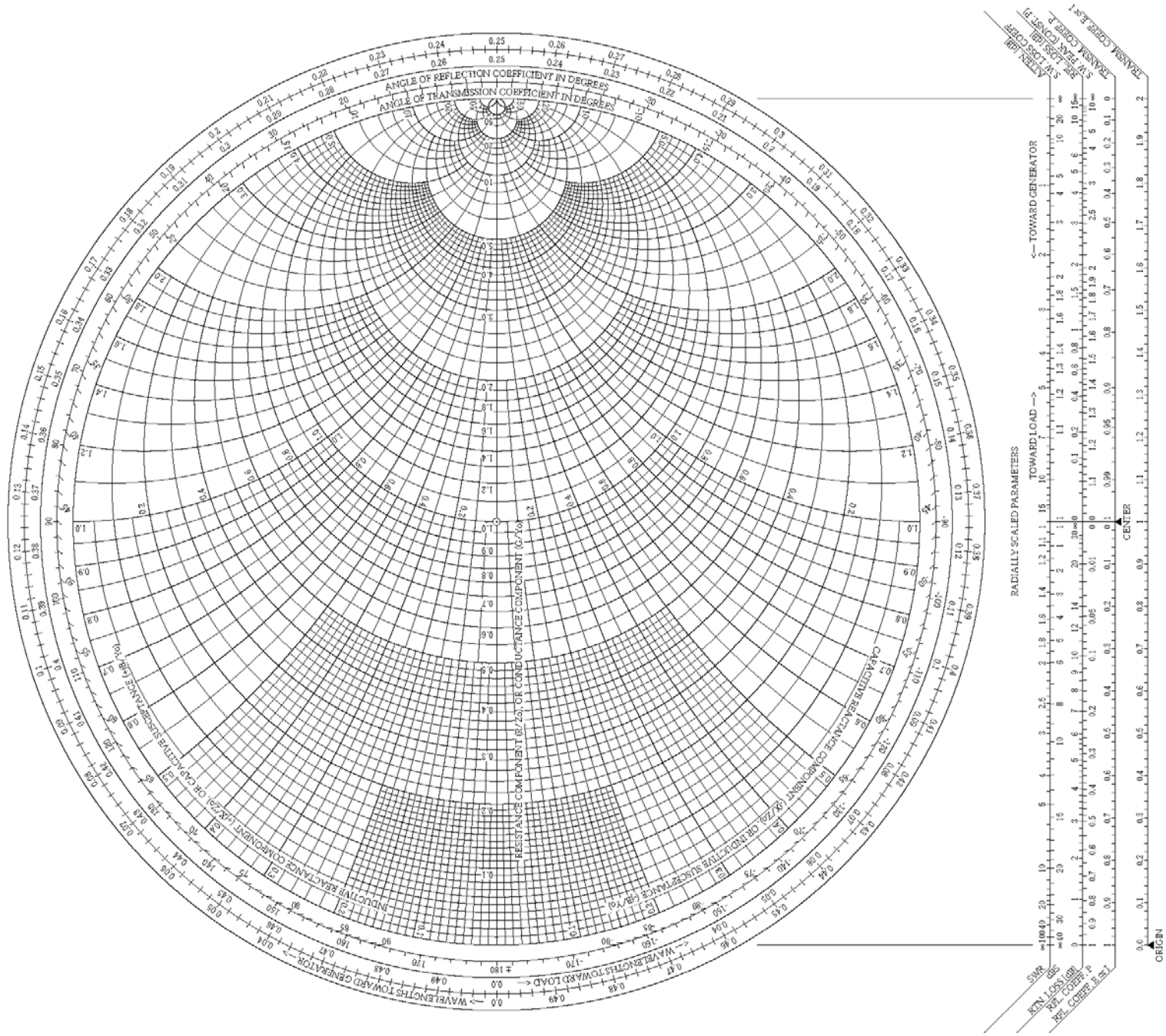

NAME	TITLE	DWG. NO.
SMITH CHART FORM ZY-01-N	COLOR BY J. COLVIN, UNIVERSITY OF FLORIDA, 1997	DATE

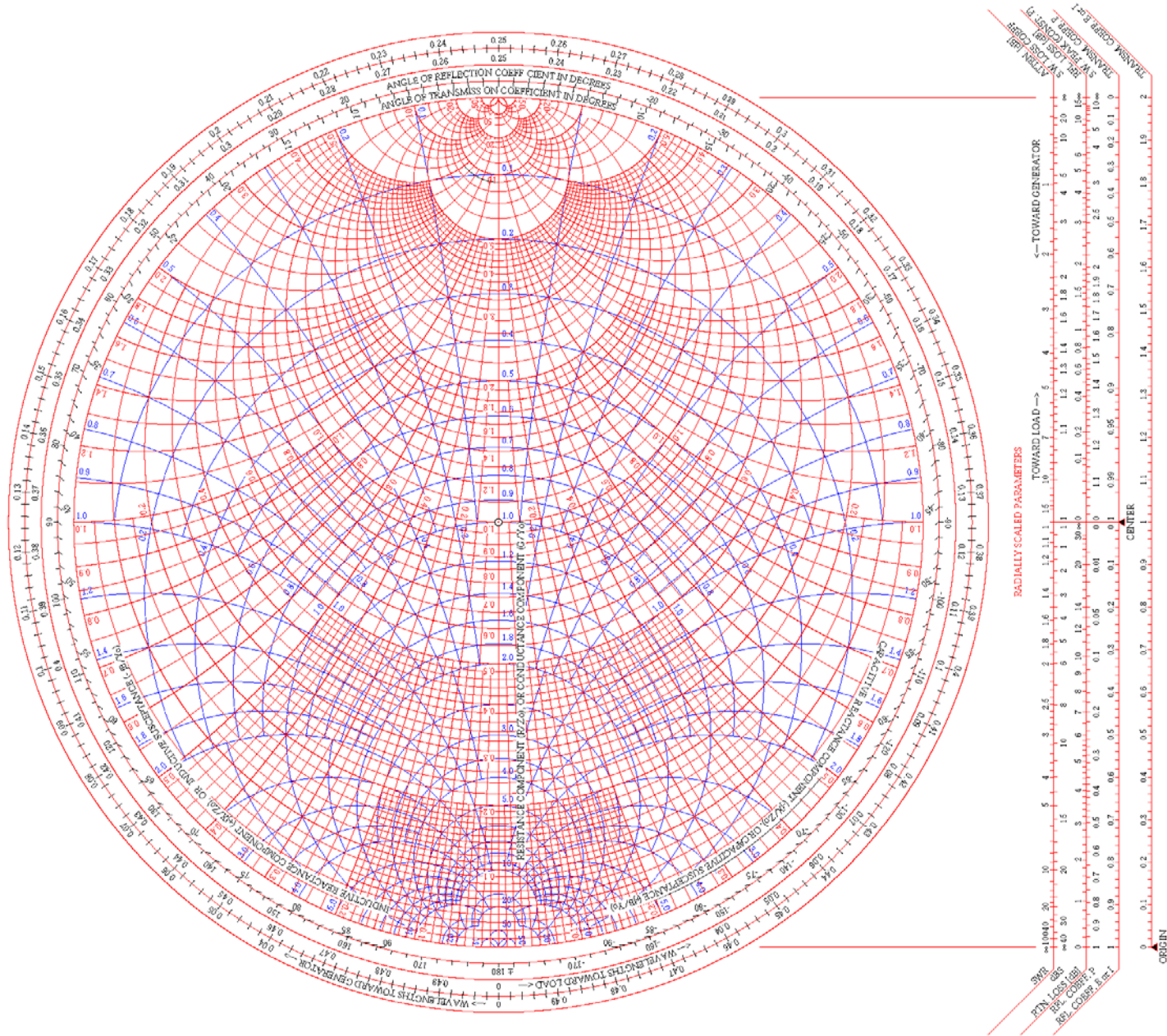NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES



Contents

- Smith Chart is a graphical aid for impedance matching using series/parallel Inductors, Capacitors and Transmission Lines
 - The Smith Chart was developed by Phillip H. Smith during the 1930s
 - Others, including Wheeler, developed similar charts
- Smith Chart based on Reflection Coefficient
- Impedance ($0 \leq R \leq +\infty$ and $-\infty \leq X \leq +\infty$), admittance, VSWR, voltage reflection coefficient (Γ), all are in “the chart”
- Live examples
- Some observations


"Smith" was a registered trademark of Analog Instruments Company, cancelled May 22, 2010

What is VSWR?


Source: www.fourier-series.com F&Rwaves

$$VSWR = \frac{V_{PEAK}}{V_{MIN}}$$

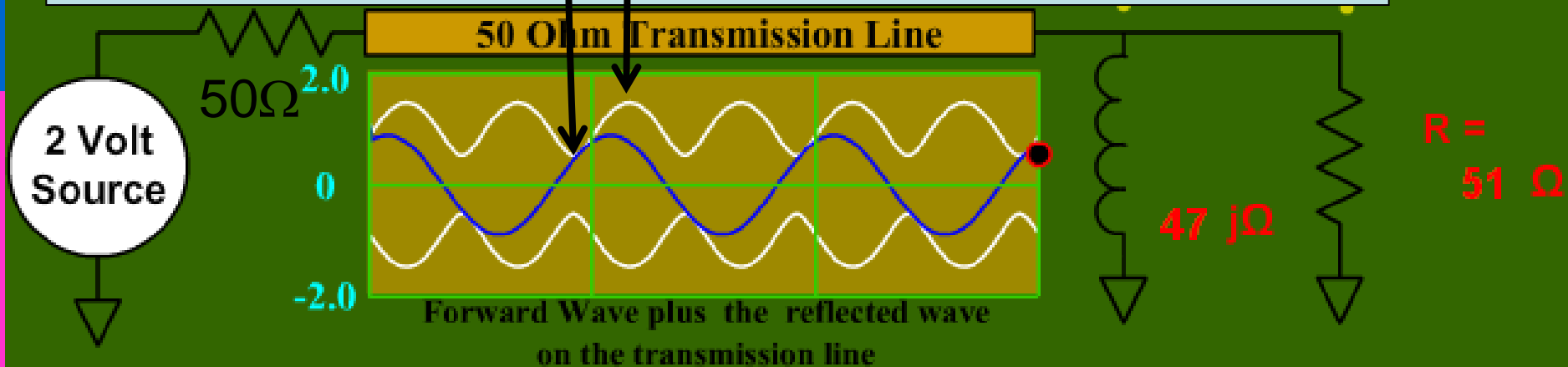Slotted lines were used in *days of auld* to measure V_{peak} and V_{min}



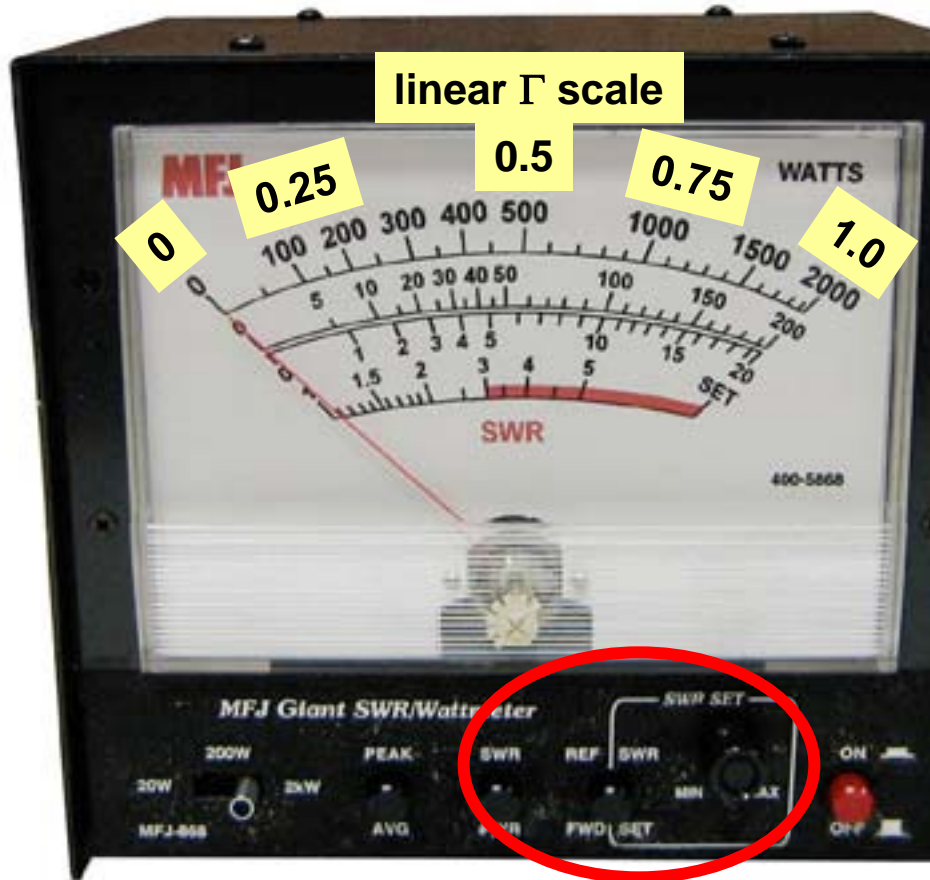What is Voltage Reflection Coefficient Γ ?



“Watt meter” is really a Directional Volt Meter with scale reading $V^2/50$ [watts]

In the “SWR” mode ...

Add a linear scale marked:

“0 to 1.0”


so ‘half scale’ = ‘half of max V’

Now instead of reading

SWR from 1 to ∞ , just read the reflection coefficient




Γ from 0 to 1 on linear scale!

VSWR on the Smith Chart

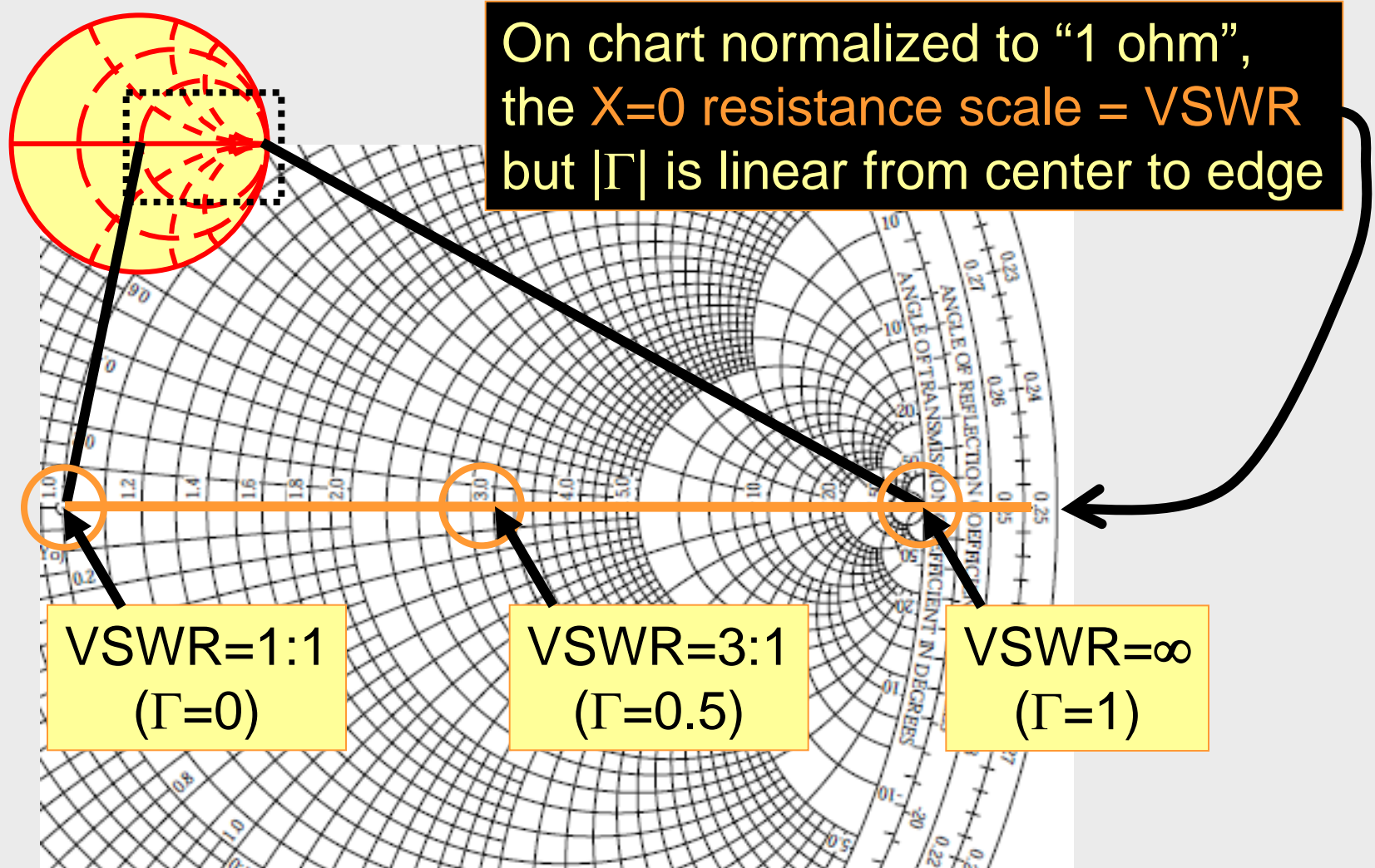


There are 3 “Circle Charts” for representing the same point

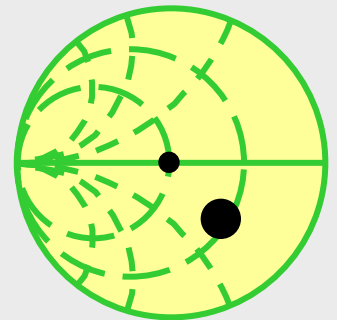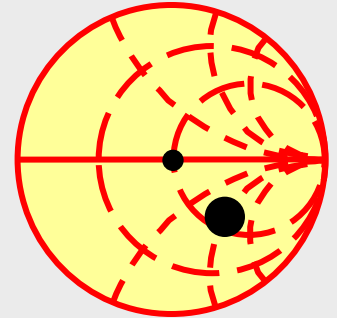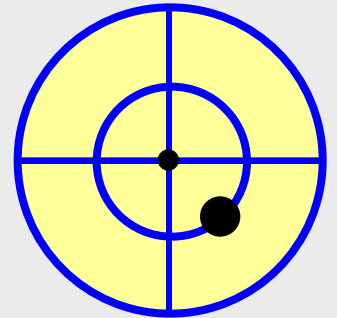- Reflection Coefficient grid, Γ for TL
 - Radius from center equals reflection coefficient magnitude and angle
- Impedance grid, $Z=R+jX$ for series LC
 - Circles of constant resistance R
 - Circle segments of constant reactance X
- Admittance grid, $Y=G+jB$ for parallel LC
 - Circles of constant conductance G
 - Circle segments of constant susceptance B



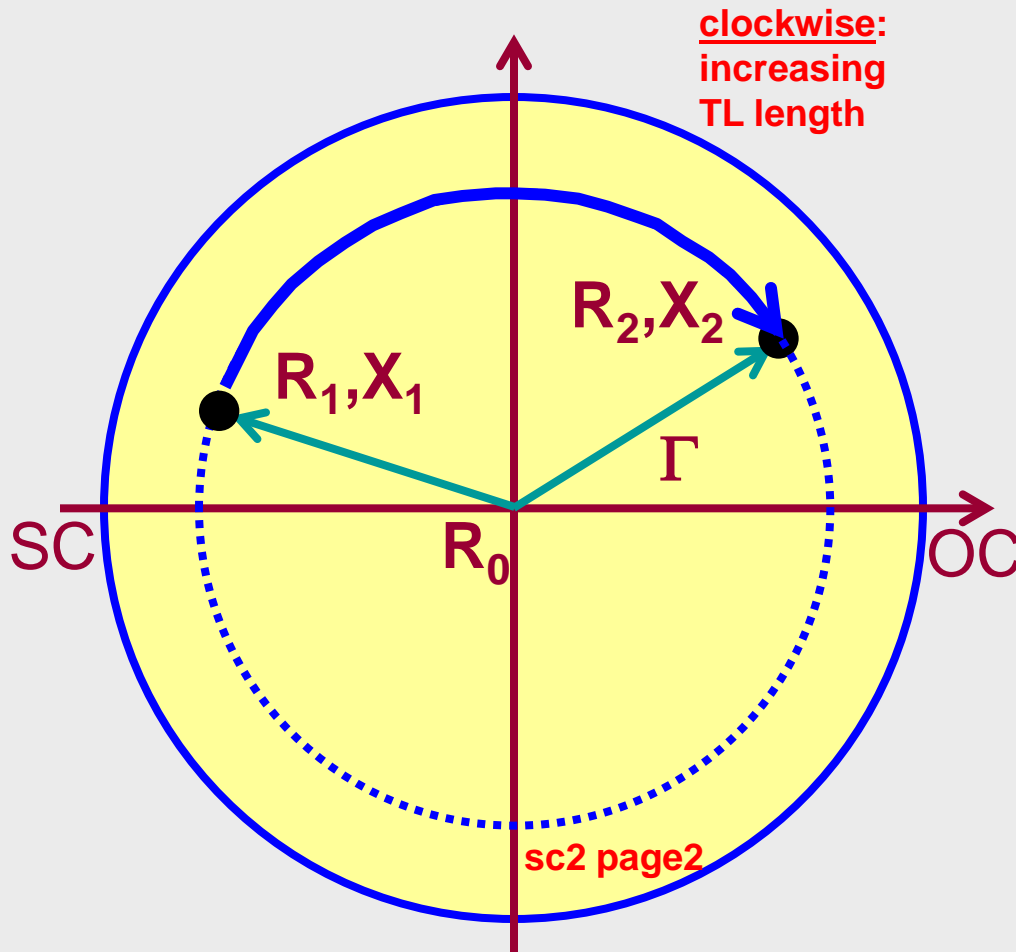
Constructing a Smith Chart: transmission line on the Γ grid




- T.L. maintains constant $|\Gamma|$ (and constant VSWR)
- Impedance is transformed
- Full circle = half a wavelength

sc3 page 1

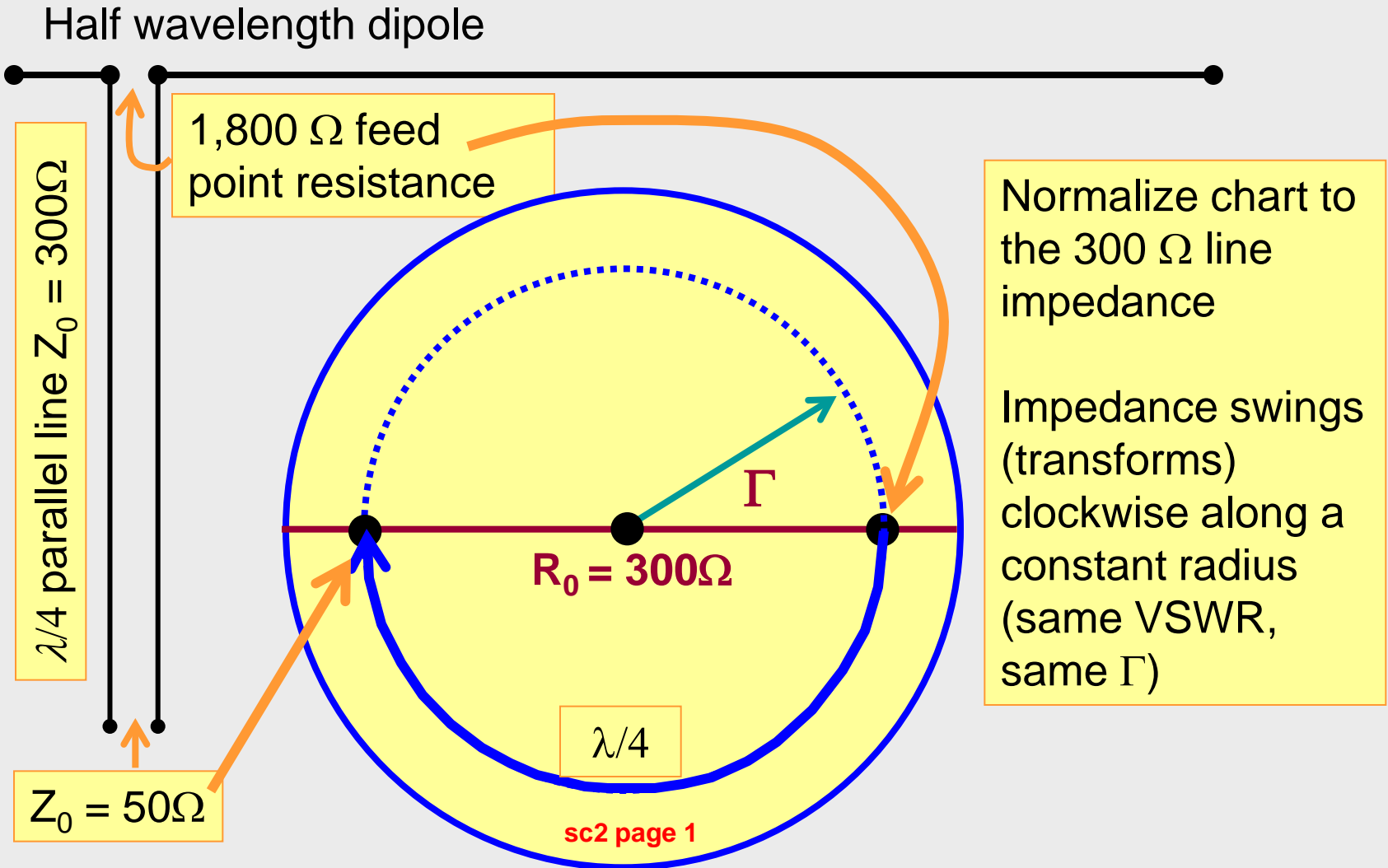Example: Match an OCF Dipole Using a Transmission Line




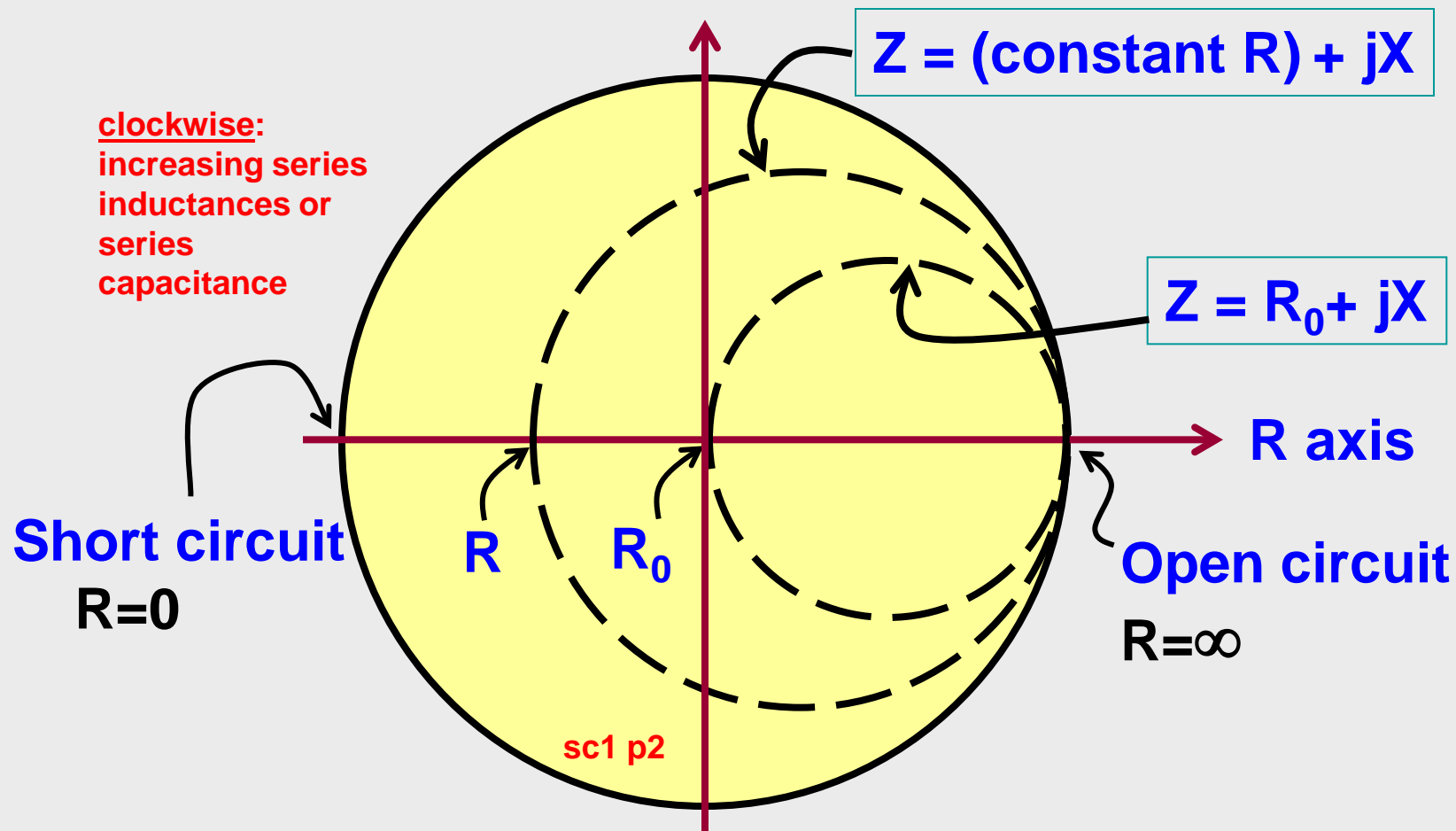Constructing a Smith Chart: constant resistance circles



Constructing a Smith Chart



constant reactance segments

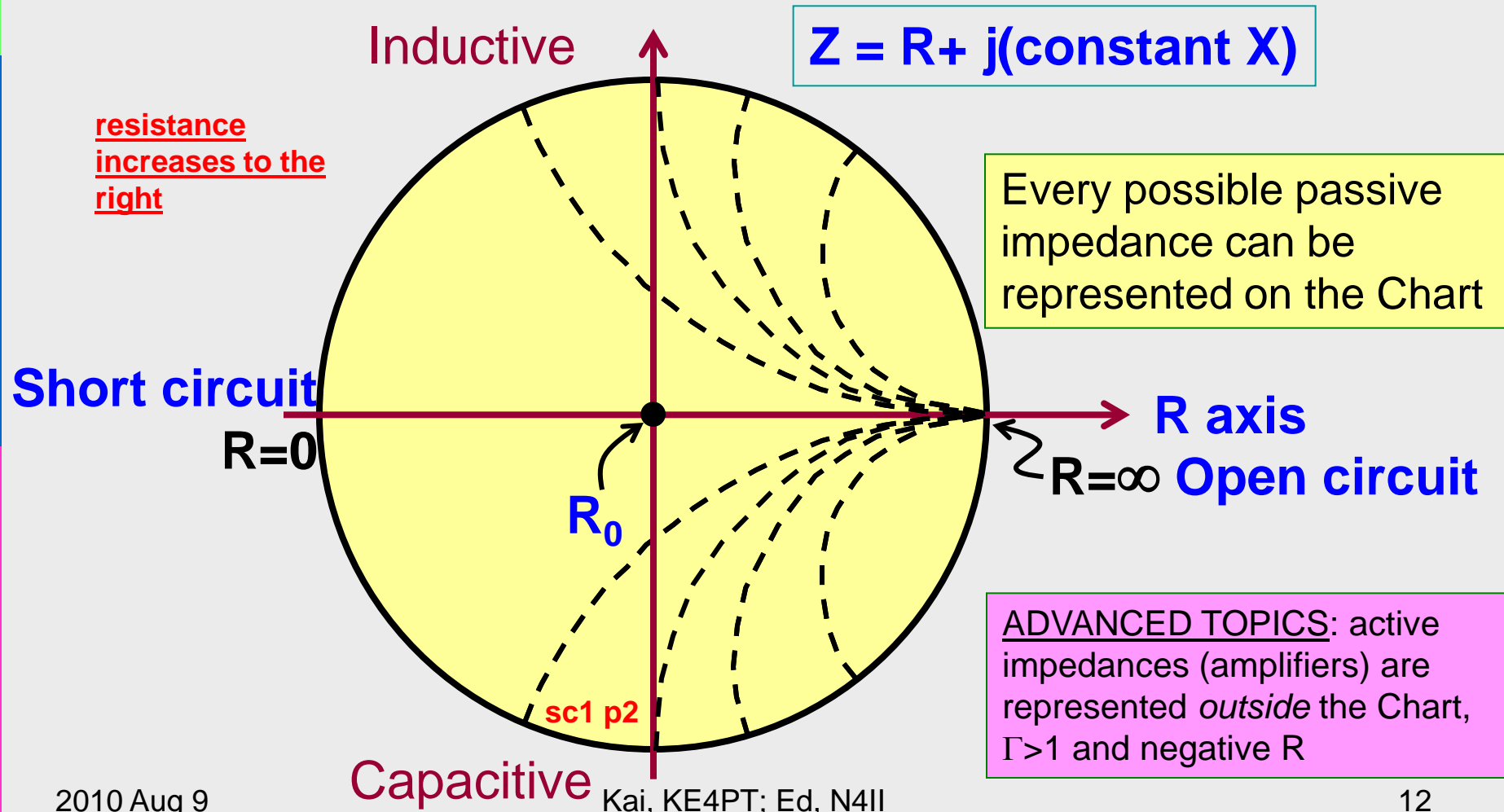

Admittance Y Chart is Mirror Image of Impedance Z Chart

constant R, constant X

constant G, constant B



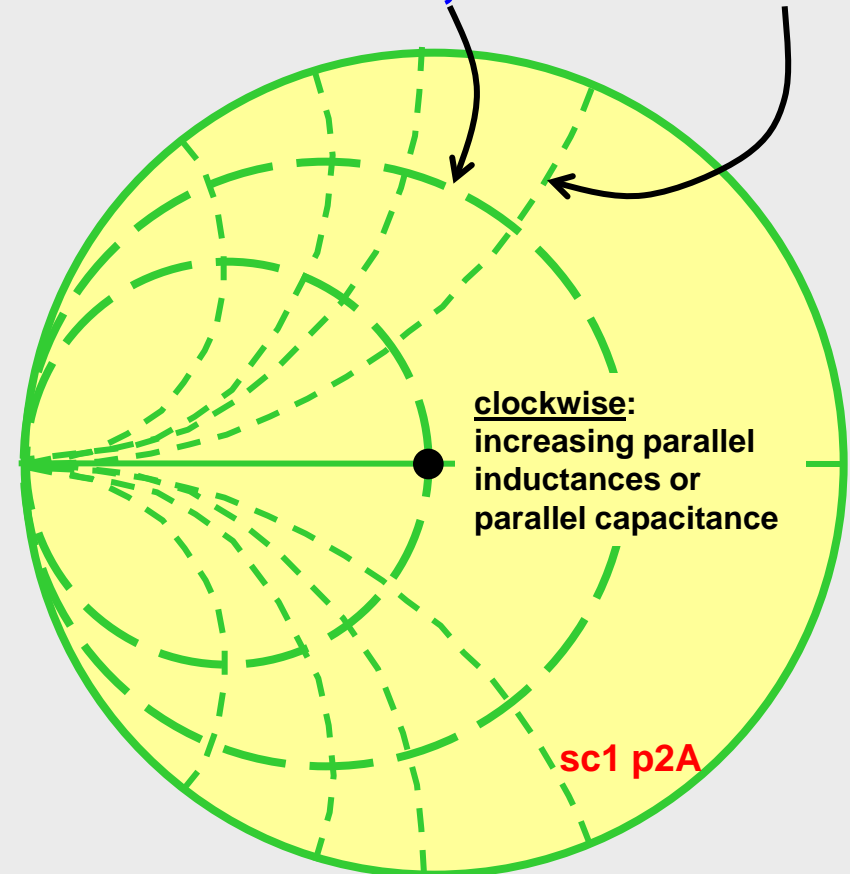
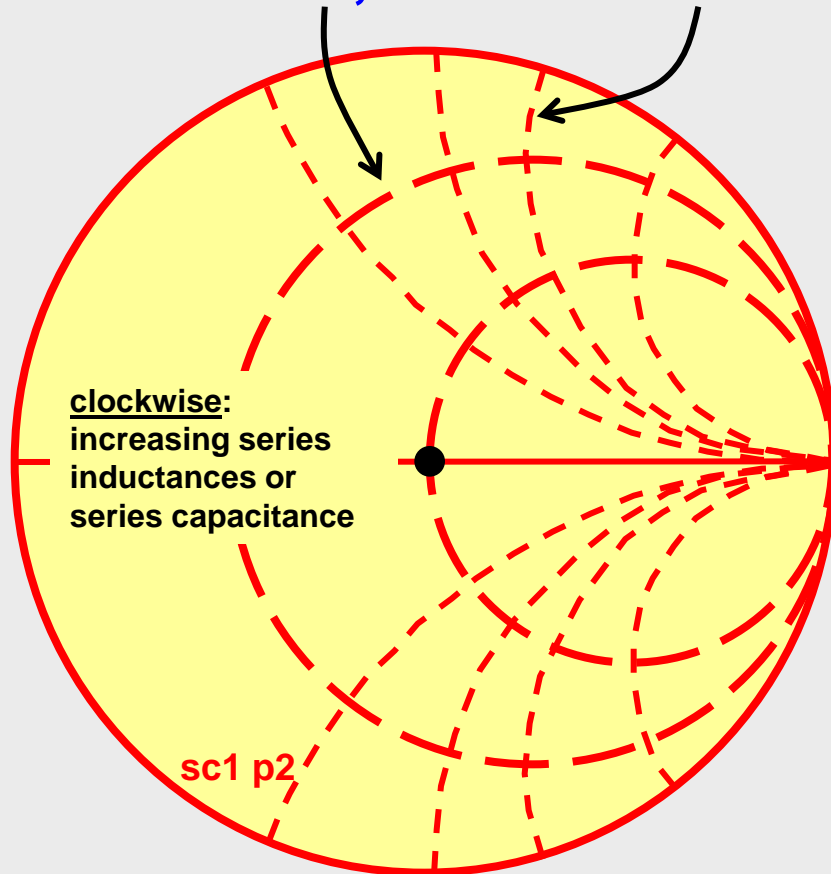


Series resistance and reactance

Parallel conductance and susceptance

Always Clockwise Movement

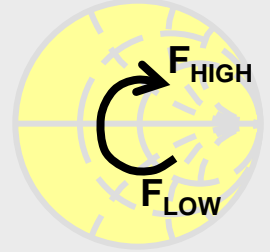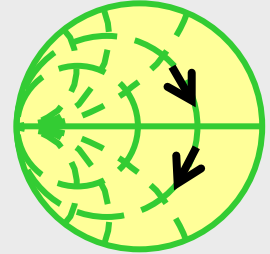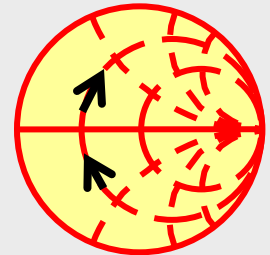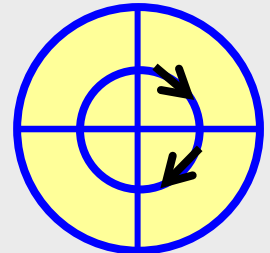- Increasing TL length moves impedance point clockwise
 - Along a constant radius
- Increasing series L(inductance) C(capacitance)
 - Moves impedance point clockwise
 - Along circles of constant resistance R
- Increasing parallel L(inductance) C(capacitance)
 - Moves impedance point clockwise
 - Along circles of constant conductance G
- Impedance vs. Frequency
 - Frequency (Hz) increases clockwise




Matching using L, C, TL, with the aid of a Smith Chart

series L,C move along the constant resistance circles, and

parallel L,C move along the constant conductance circles, and



transmission lines move along a constant radius,

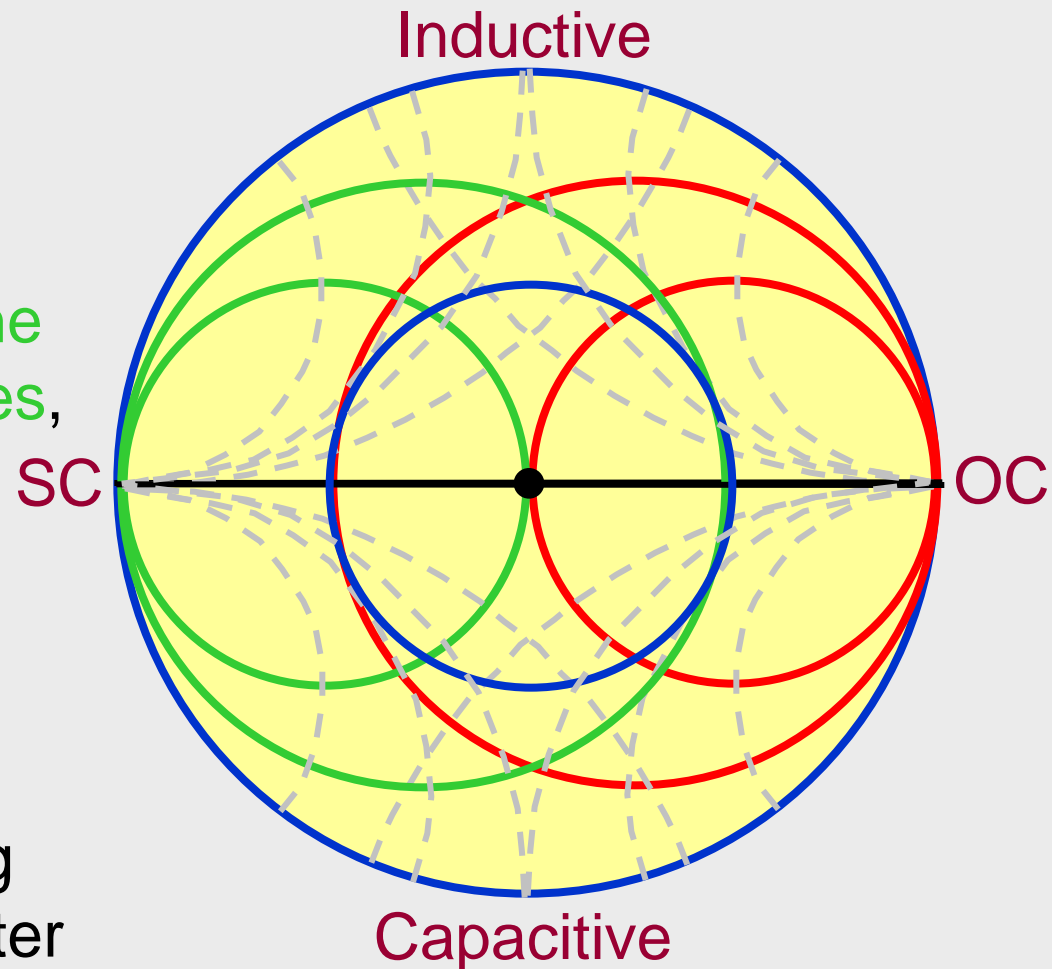goal: move *clockwise* along the circles to reach the center




Antenna impedances are matched by tuner one frequency at a time

AH-4 component range:

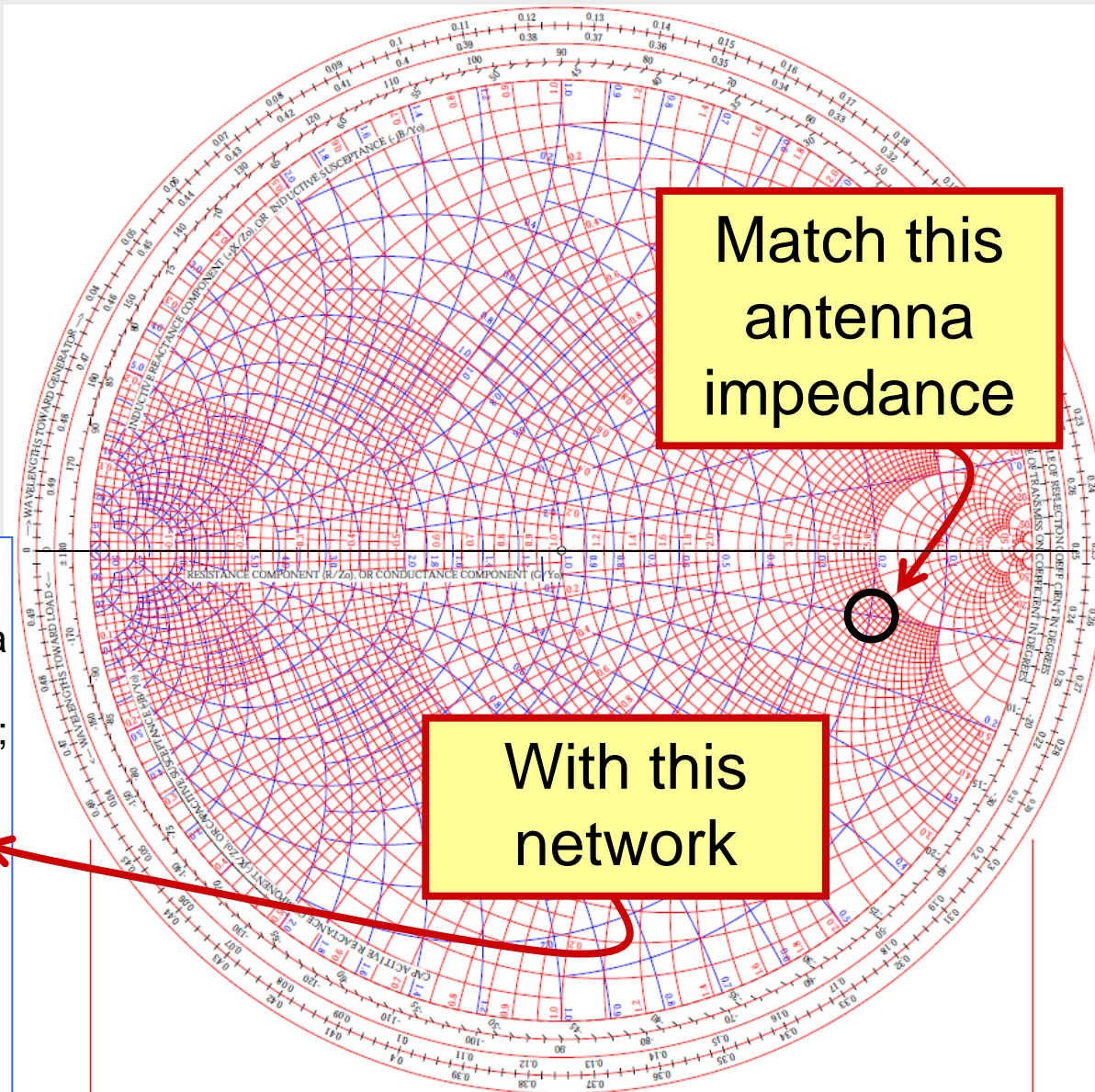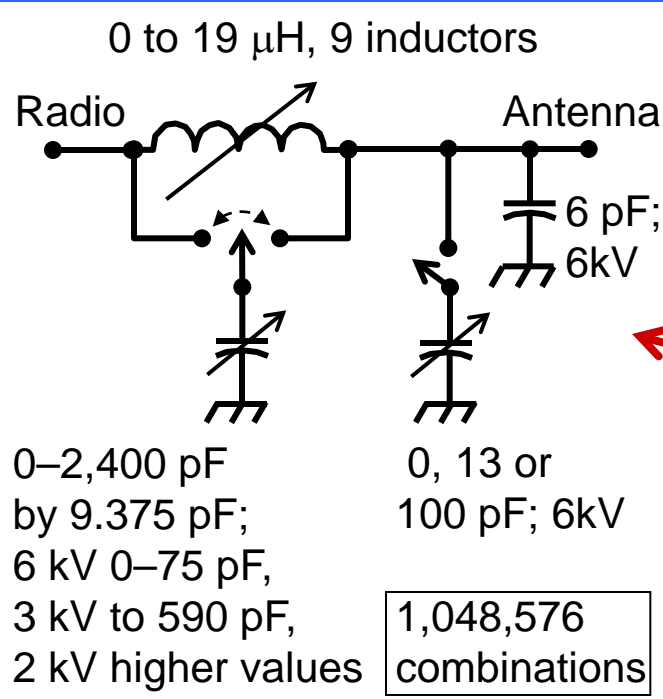

Generated by 4nec2
<http://home.ict.nl/~arivoors/>

Choose a Network Topology

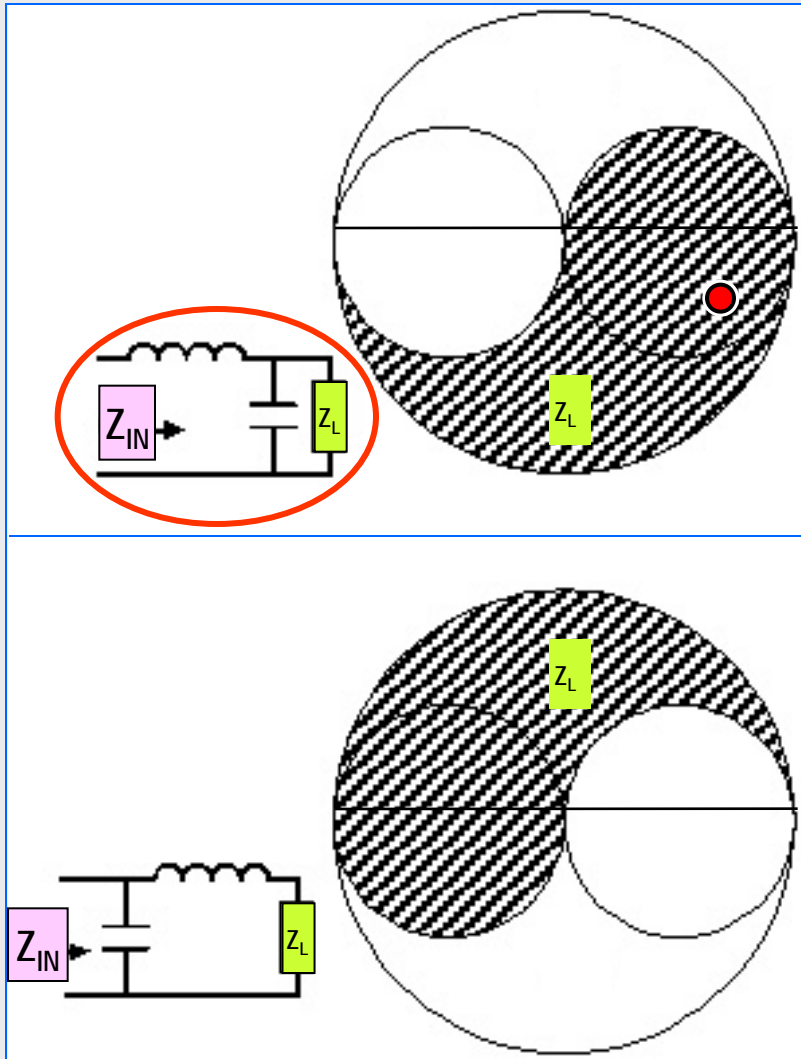

Which way?
Parallel capacitor on load side
or input side?



Load impedances in the
shaded region can be matched
with the network topology
shown on the left

ADVANCED TOPICS: the
range of L and C determines
how much of shaded area can
be matched.

After: V.Iyer, QuickSmith analysis software,
<http://www.nathaniyer.com/qsdw.htm>

Tuner uses 2
variable
elements to
match within
 $VSWR < 1.5$
Goal circle

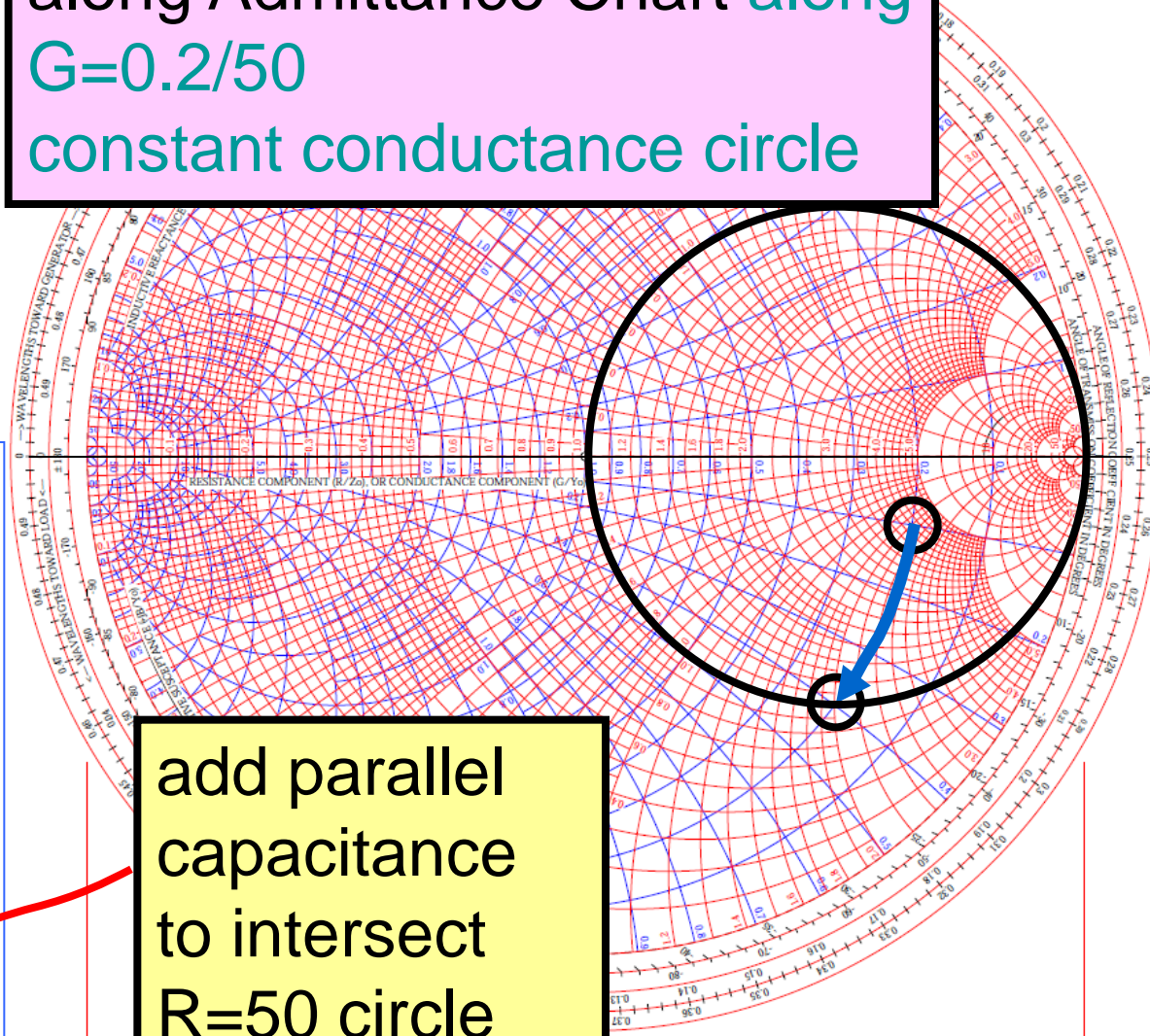
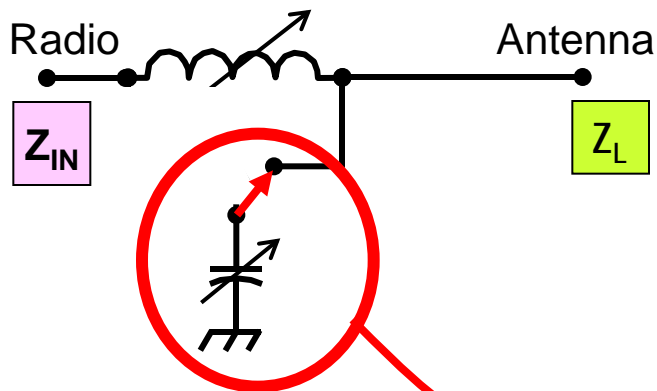
parallel reactance moves
along Admittance Chart **along**
 $G=0.2/50$
constant conductance circle



add parallel
capacitance
to intersect
 $R=50$ circle

Tuner uses 2
variable
elements to
match within
 $VSWR < 1.5$
Goal circle

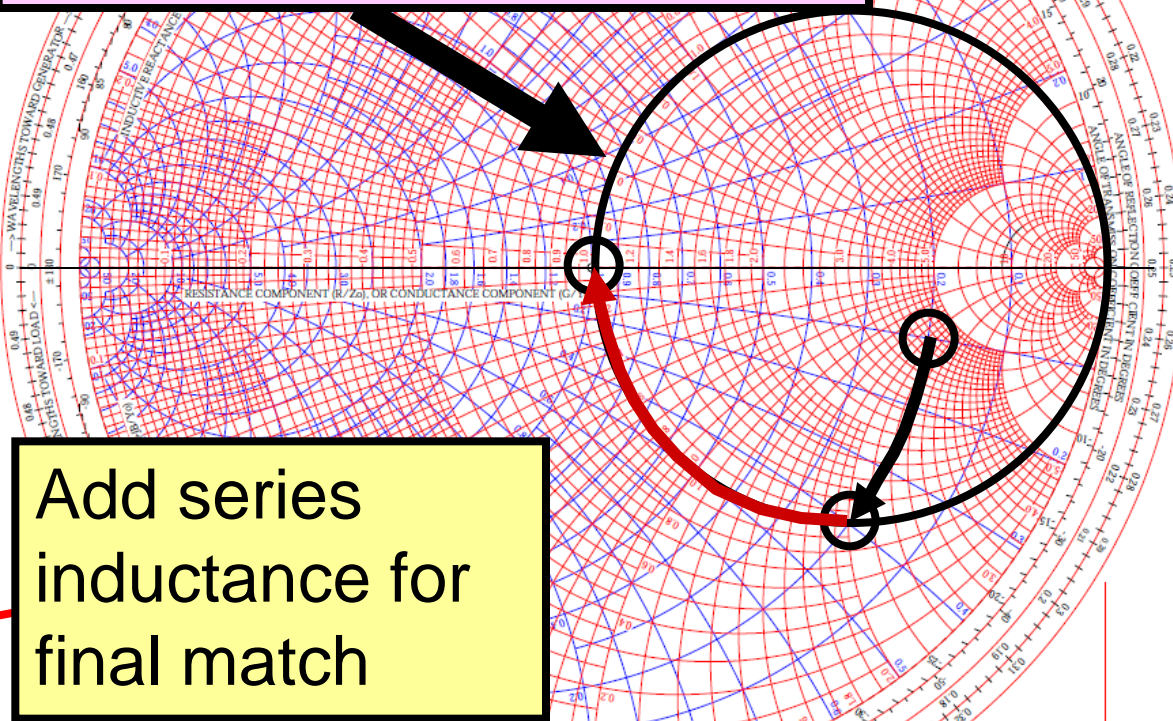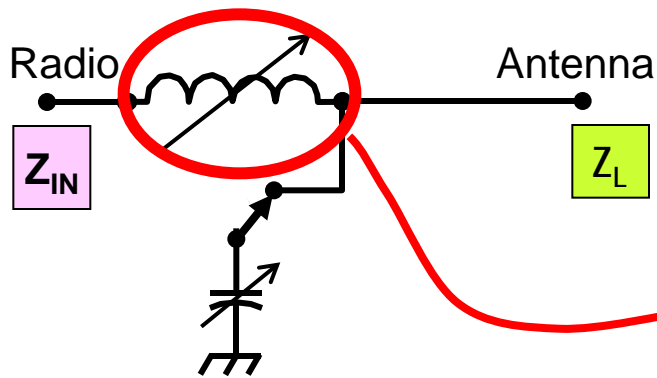Series reactance moves
along Impedance Chart
 $R=50$ ohm
constant resistance circle




Add series
inductance for
final match

ADVANCED TOPICS: this
answer is not unique! Other
solutions are be possible.

Component Values at f=21MHz

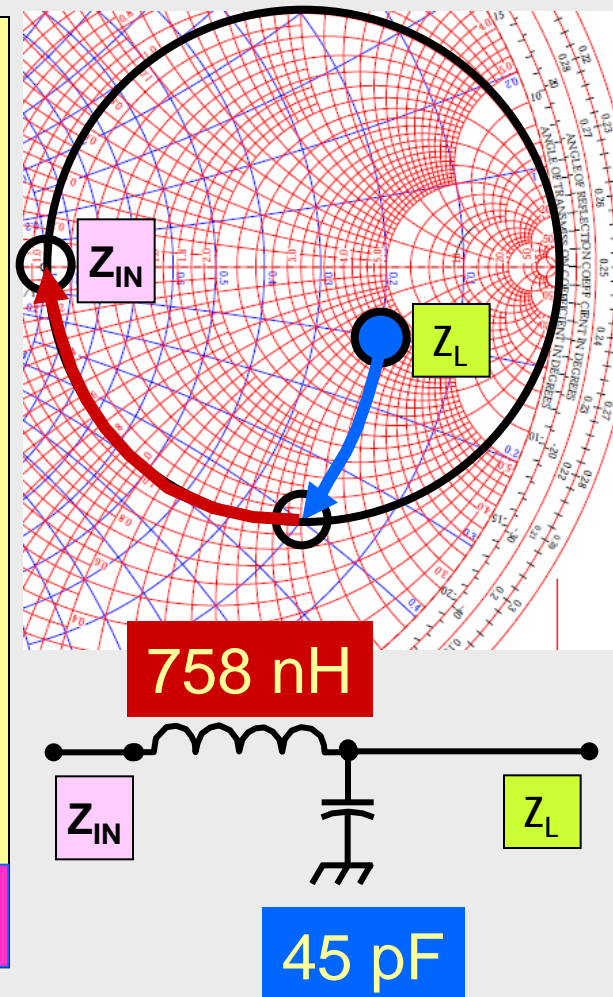- Starting at $1/Z_L = 1/(200-j100) = Y = (0.2+j0.1)/50$
- Parallel capacitor to get to $Y = (0.2+j0.4)/50$
- $C = (0.4-0.1)/(50 \times 2\pi f) = 45 \text{ pf}$
- $Z = 1/Y = (1-j2)50 = (50-j100)$
- Series $L = 100/2\pi f = 758 \text{ nH}$




Matching over a Bandwidth

- Impedance vs. frequency trace moves in a clockwise direction
- An ideal match at mid frequency is not the same as a band – optimized match

ADVANCED TOPICS:

Optimization can be done over a bandwidth; different criteria yield different results


Mid-band Single-tuning Matching

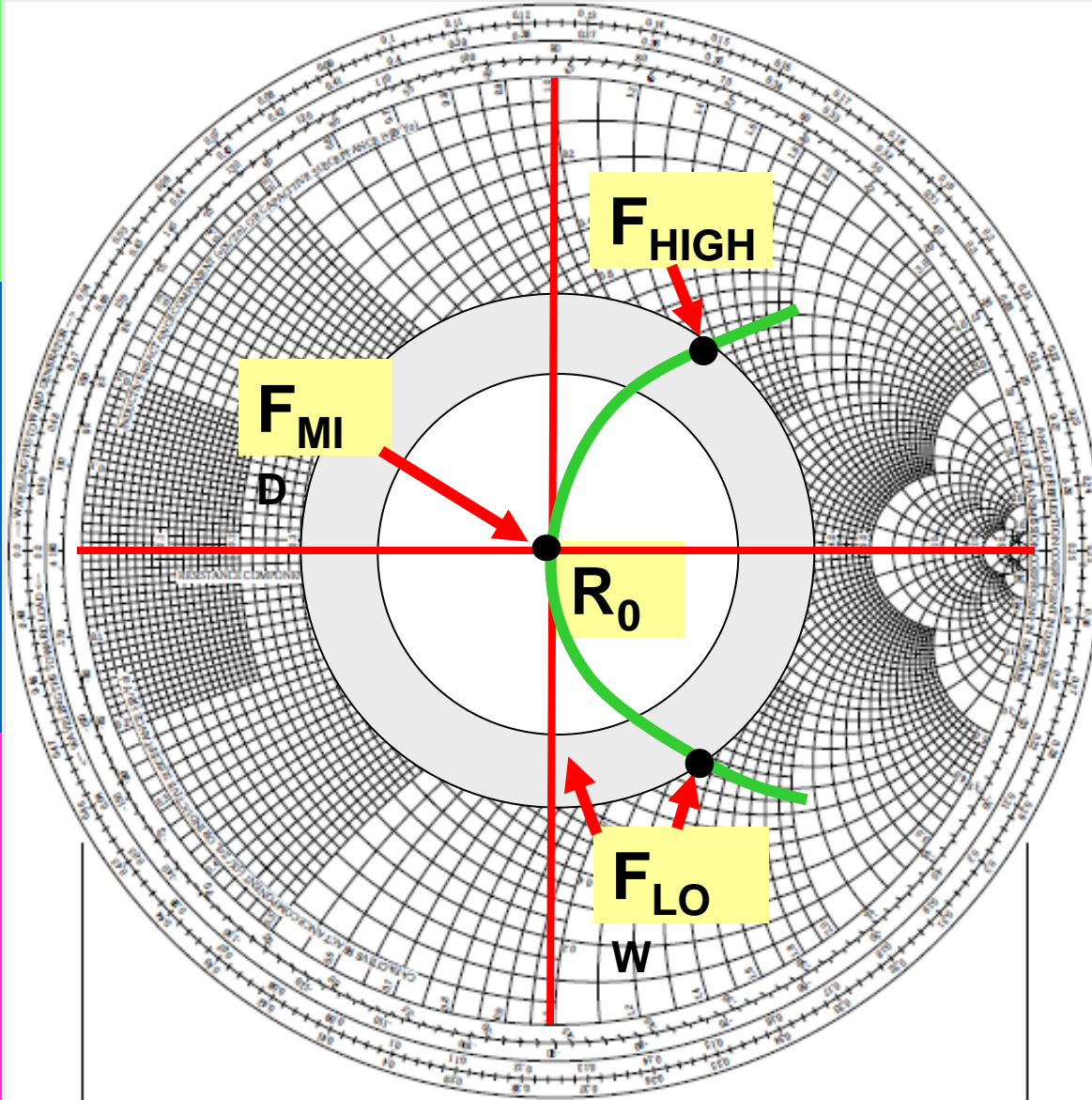

- Midband match – F_{HIGH} and F_{LOW} are outside the white VSWR goal circle
- Mid band is perfectly matched, but band edges are out of spec

ADVANCED TOPICS: answer not unique: match can be optimized for best mid band match or best bandwidth

Optimum BW Single-tuning Matching

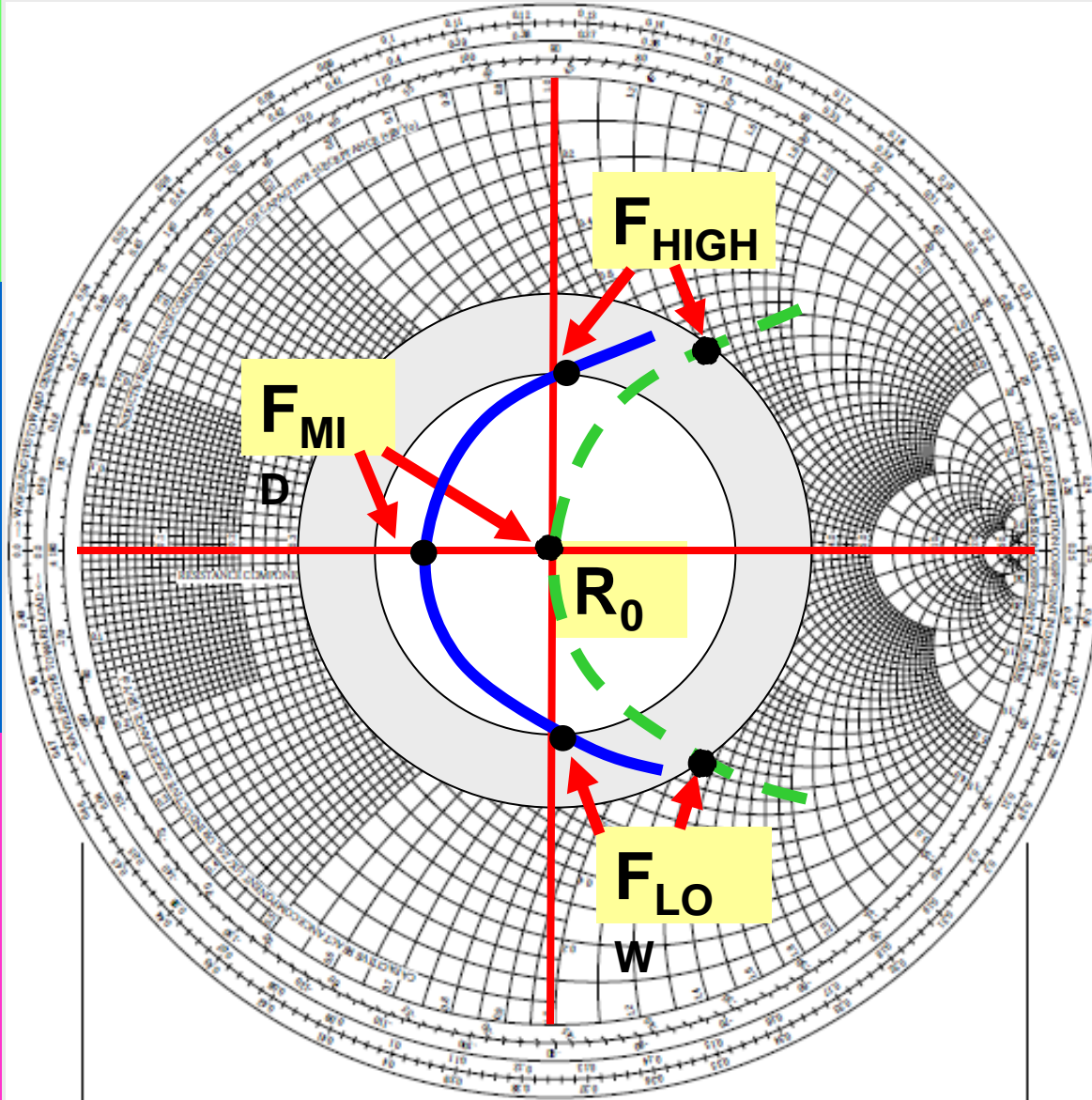

- Midband match – F_{HIGH} and F_{LOW} are outside the VSWR goal circle
- Wheeler Band Edge minimum VSWR tuning – F_{HIGH} and F_{LOW} on vertical axis, has best BW

Resources: <http://www.fourier-series.com>

- [Reflection.swf](#)
 - Reflection and transmission coefficient
- [smithchart1.swf](#)
 - Mapping resistance and reactance
- [smithchart2.swf](#)
 - Adding a transmission line
- [smithchart_L_C_match.swf](#)
 - Parallel and Series equivalent
 - Match Circuit with 2 lumped elements
- [smithchart3.swf](#)
 - Transmission line, and matching stub
- [smithchart4.swf](#)
 - T.L. and a series/parallel element
 - Relation to circuit element

More Resources:

- QuickSmith, by V. Iyer, Smith Chart based linear circuit simulation software program for Microsoft Windows
 - <http://www.nathaniyer.com/qsdw.htm>
- "How does a Smith Chart Work?" Rick Nelson, Test and Measurement World, July 2001
 - http://www.sss-mag.com/pdf/smith_chart_basics.pdf
- Images of a Smith Charts:
 - Impedance: <http://www.sss-mag.com/pdf/smithchart.pdf>
 - Immittance: http://rfic.ucsd.edu/files/smith_chart.pdf
- "ARRL Radio Designer and the Circles Utility Part 1: Smith Chart Basics", W. E. Sabin, WØIYH: QEX, Sept/Oct 1998, pp.3-9
 - http://www.sss-mag.com/pdf/arrl_circles.pdf

Summary

- Smith Chart – a graphical tool for matching
- Combinations of transmission lines, series/parallel inductors/capacitors are used
- Examples illustrate some matching uses of the Smith Chart
- Best match over a bandwidth and perfect match at one frequency are not the same!
- See 'Resources' for additional information
- Advanced topics: $-R$ = amplifier, outside chart; optimization vs. frequency; range of matching components; using TL stubs

Extra Slides

VSWR is an Obsolete Holdover from the days of slotted line measurements

$$VSWR = \frac{V_{PEAK}}{V_{MIN}} = \frac{V_{FORWARD} + V_{REFLECTED}}{V_{FORWARD} - V_{REFLECTED}}$$

$$\Gamma = \frac{V_{REFLECTED}}{V_{FORWARD}}$$

We actually measure and use reflection coefficient Γ

Impedance Z , Admittance Y and Reflection Coefficient Γ are Related

- Each point can be expressed in three ways: Z , Y , and Γ
- All impedances and admittances fall inside $\Gamma=1$ circle
- VSWR relates to the *magnitude* of reflection coefficient $|\Gamma|$
- *Reactances (susceptances)* convert to inductors and capacitors

$$\Gamma = \frac{Z - Z_0}{Z + Z_0} = \frac{Y_0 - Y}{Y_0 + Y}$$


$$Z = \frac{1}{Y}$$

$$|\Gamma| = \frac{VSWR - 1}{VSWR + 1}$$

$$C = \frac{1}{2\pi f X_{CAP}}$$


$$L = 2\pi f X_{IND}$$

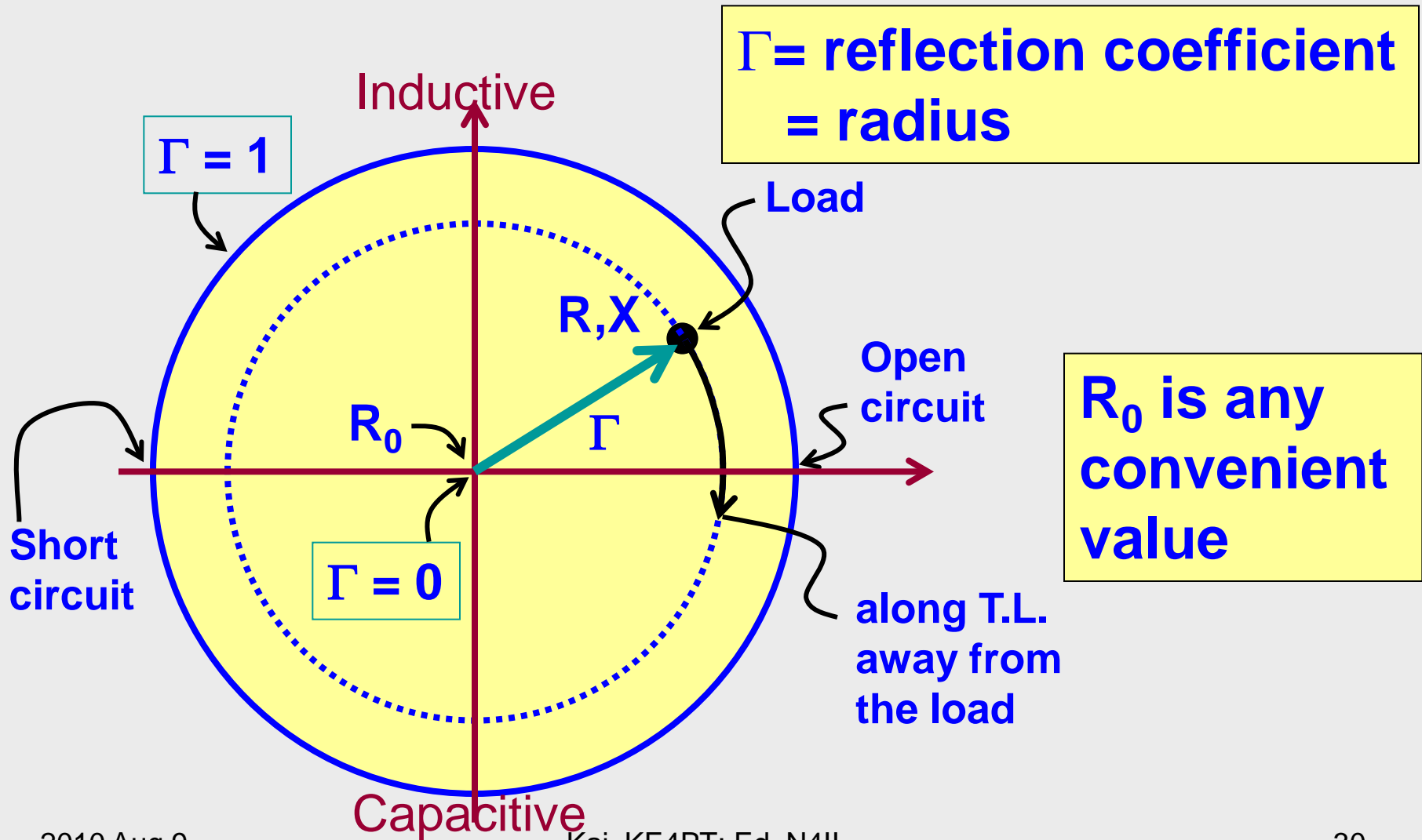Constructing a Smith Chart: the *reflection coefficient grid*




Impedances and un-tunable range

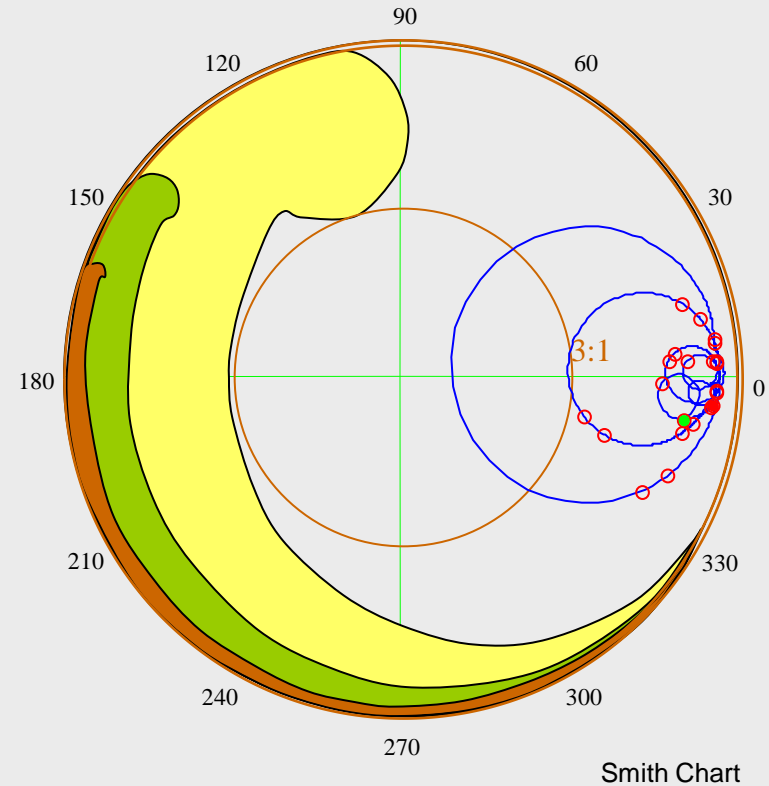- A coupler matches any impedance, except for a crescent shaped region, in the left extreme of the Smith chart
- As you operate lower in frequency, this un-tunable crescent becomes larger; and an un-tunable region at the outer radius of the Smith chart begins to grow



AH-4 component range:

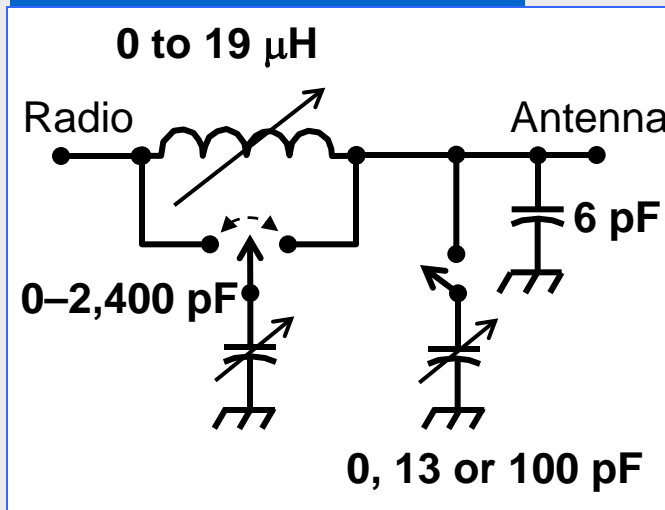

For the AH-4 parts range:

Not tunable below 7.0 MHz

Not tunable below 4.0 MHz

Not tunable below 1.8 MHz