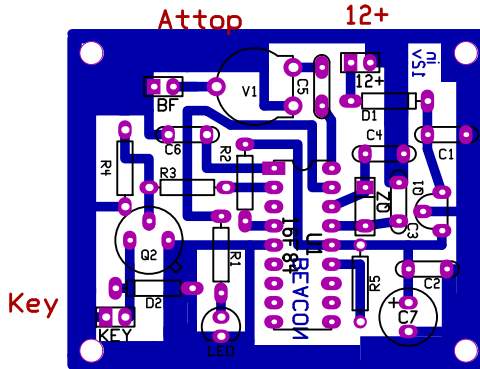


Beacon composto QRSS3 formato dal
programma, la pausa 15" secondi



IK1HGI BEACON 2007

R1 470 ohm
R2 33k ohm
R3 10k ohm
R4 100k ohm
R5 5k6 ohm

C1 100nF
C2 100nF
C3 22pF
C4 22pF
C5 10nF
C6 100nF
C7 47uF 25
D1-2 1N4002
Q2 BC108 similar
Quarzo 4 MHZ
Q1 78L05
U1 16F84
Led rosso
V1 10k trimer