
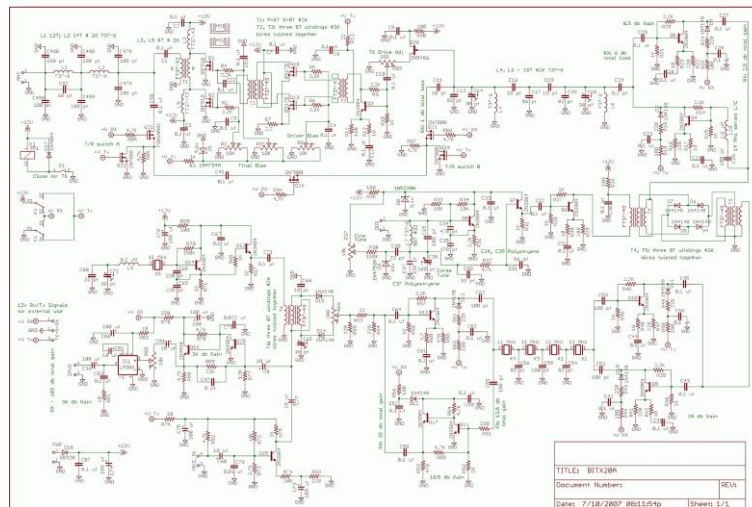


On1mws SSB transceiver.

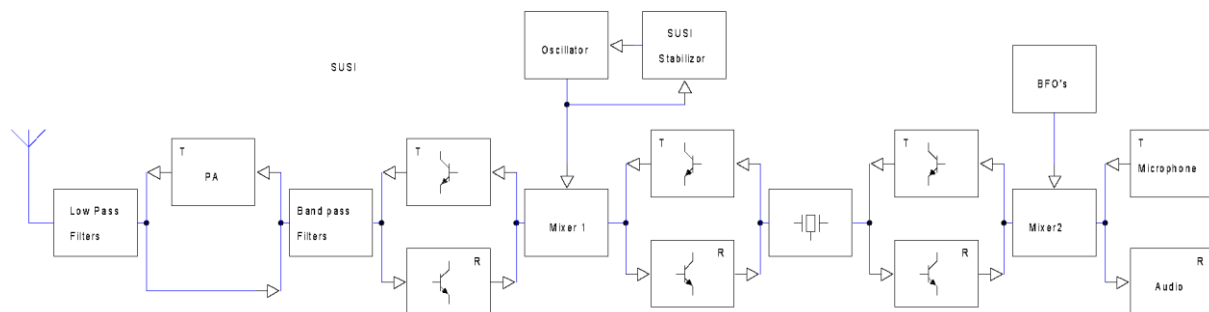



The transceiver is based on the 2007 Bitx20A (above) I immediately like the bi-directional circuit. What I also like is that the circuit uses readily available cheap components. Many links on the net describe how the circuit works. Later on, I based other rigs on the BITX20A circuit and found it is easy to build for the average homebrewer and pretty good in performance. Much better than any NE602/LM386 circuit.


My version is all-band. Also, it features another audio circuit and a different oscillator with SUSI stabilization.



80M to 20M=downconversion, 17M to 10M=upconversion.

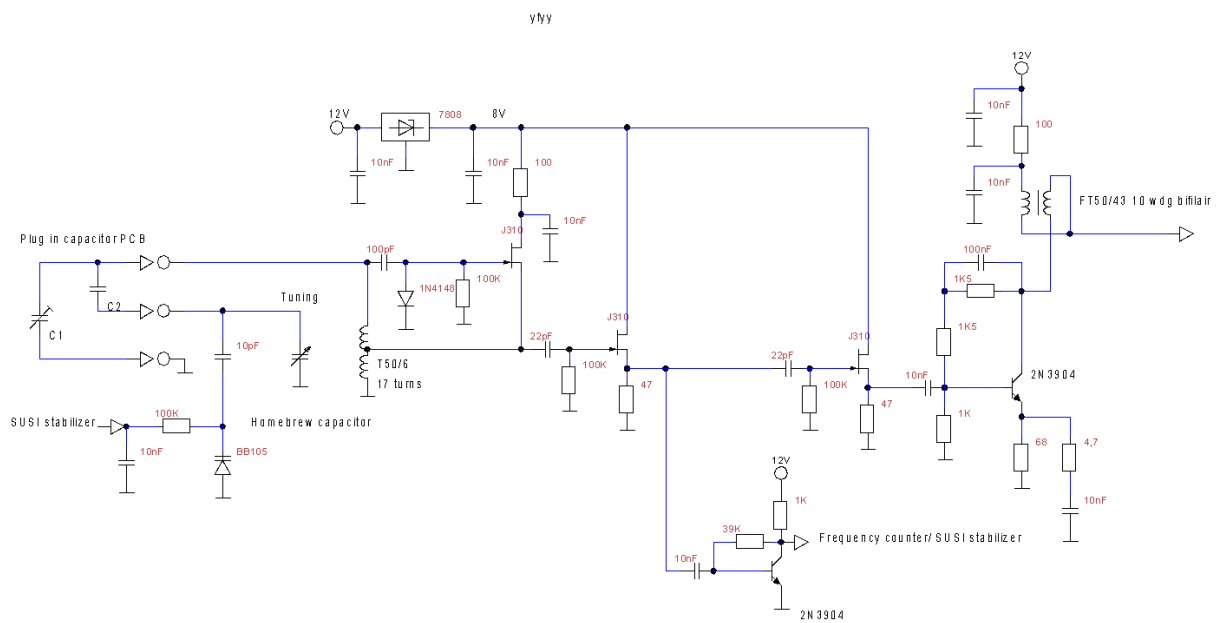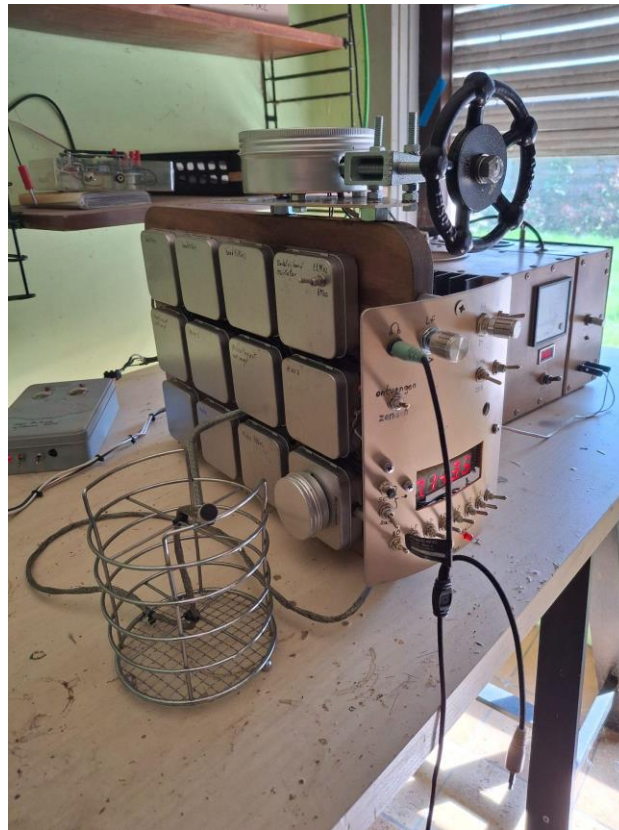To avoid an oscillator that needs to run on high frequencies, the upper bands are upconversion instead of the usual downconversion. So far I can only claim QSO's on 40 and 20M and one QSO on 80M. It should work on the higher bands but I don't have a antenna to do it. This project is soldered in tin boxes and discarded 'normal' enclosures.



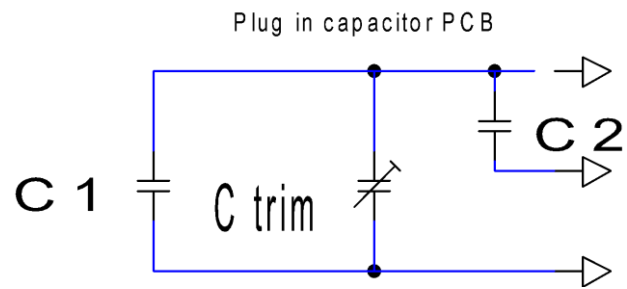

Tuning bandsread is always about 300KHZ.

	Ctrim	C1	C 2	Frequency +-	IF
80 and 12M	40p	47p	47p	14,5MHz	11 Mhz
40 and 10m	40p	/	10p	18Mhz	11 Mhz
20M	22p	/	5p	25MHz	11 Mhz
17M	60p	220p	470p	7MHz	11 Mhz
15M	40p	47p	47p	13Mhz	8 Mhz

The oscillator features a homebrew tuning capacitor.




The hot side of the capacitor is a steel tube with an inner diameter of 12mm. The ground is a M8 threaded rod. As the rod gets turned in or out the tube, the capacitance changes. The capacitance is

about 10pF. The rod is driven through a steel beam bracket. This bracket has two M8 holes on both sides. The bracket provides a 54:1 gear ratio.




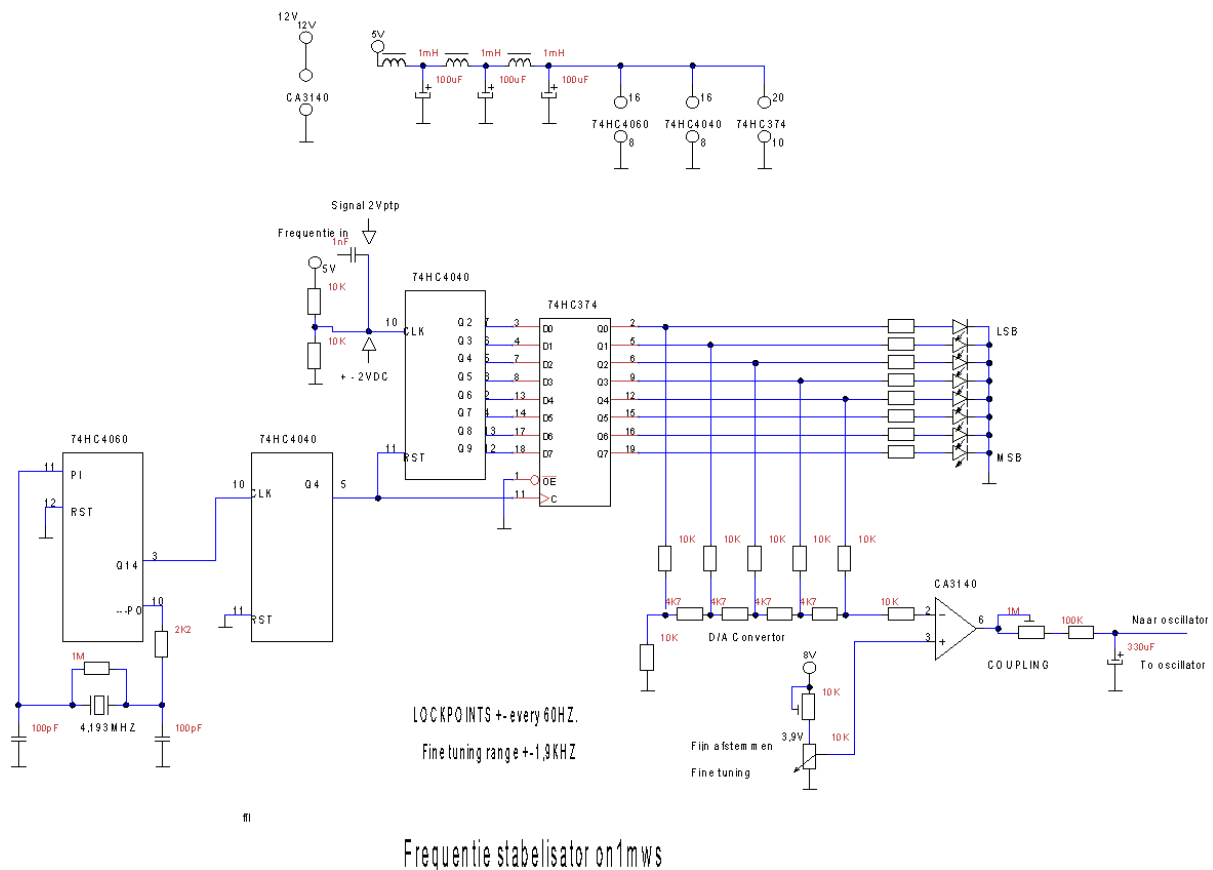The homebrew capacitor works very well. It is just as good as a commercial one but a lot cooler.




This stabilizer is described in my opinion easier to build than a Huff and Puff stabilizer and also superior. A discription of the circuit given in another PDF. The lockpoints are spaced about 60HZ apart. Link below.


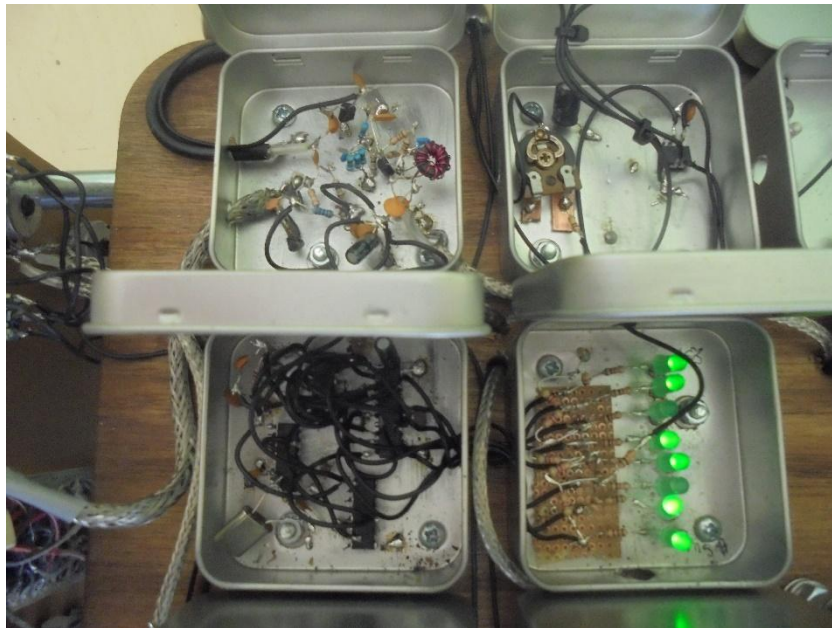
<https://www.qsl.net/on1mws/frequentie%20koppelus.pdf>





Frequency counter dl4yhf.

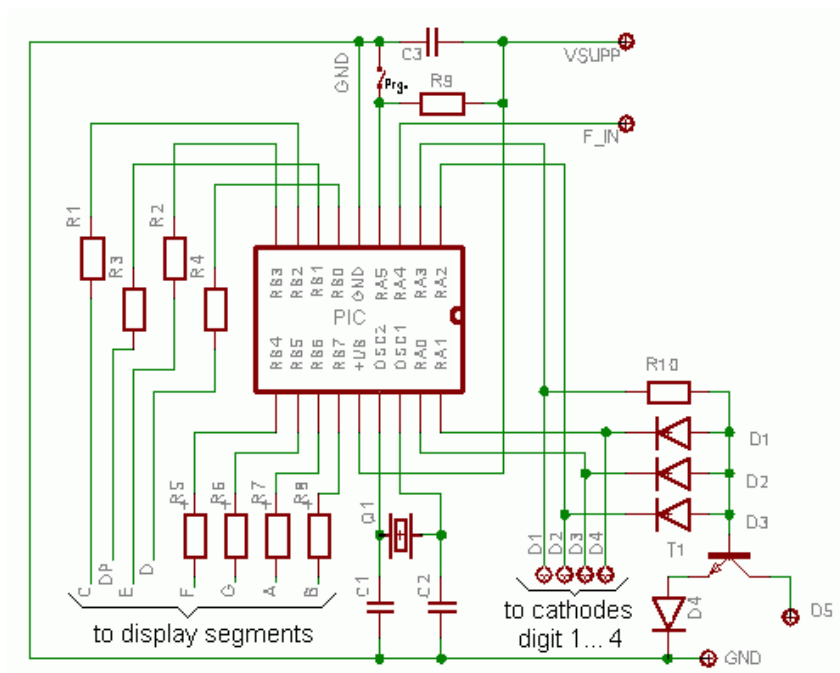

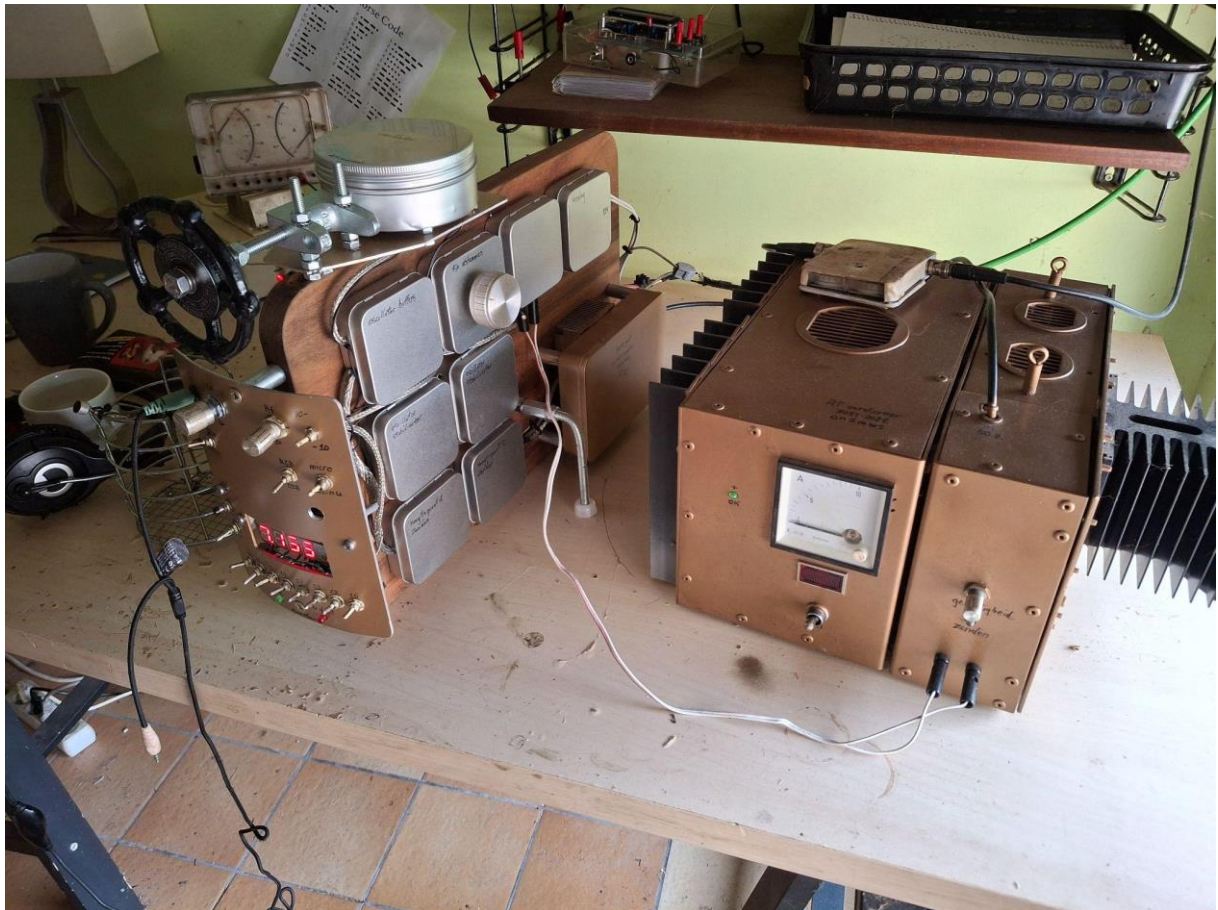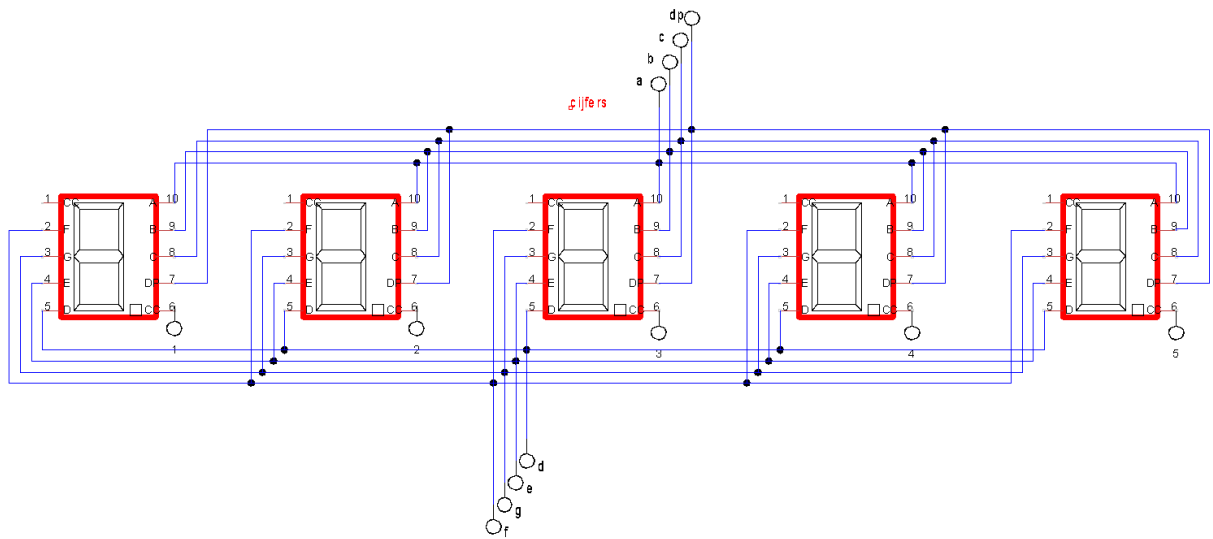
Component values for variant 2 (as shown above): R1...R8 = 1k, R9=R10=10k, D1..D4=1N4148, T1=BC547 or similar, C1=C2 about 22pF (select them to tune the crystal to exactly 20 MHz), C3=100nF, Q1=20 MHz, PIC: 16F628 programmed with firmware "counter2.hex".



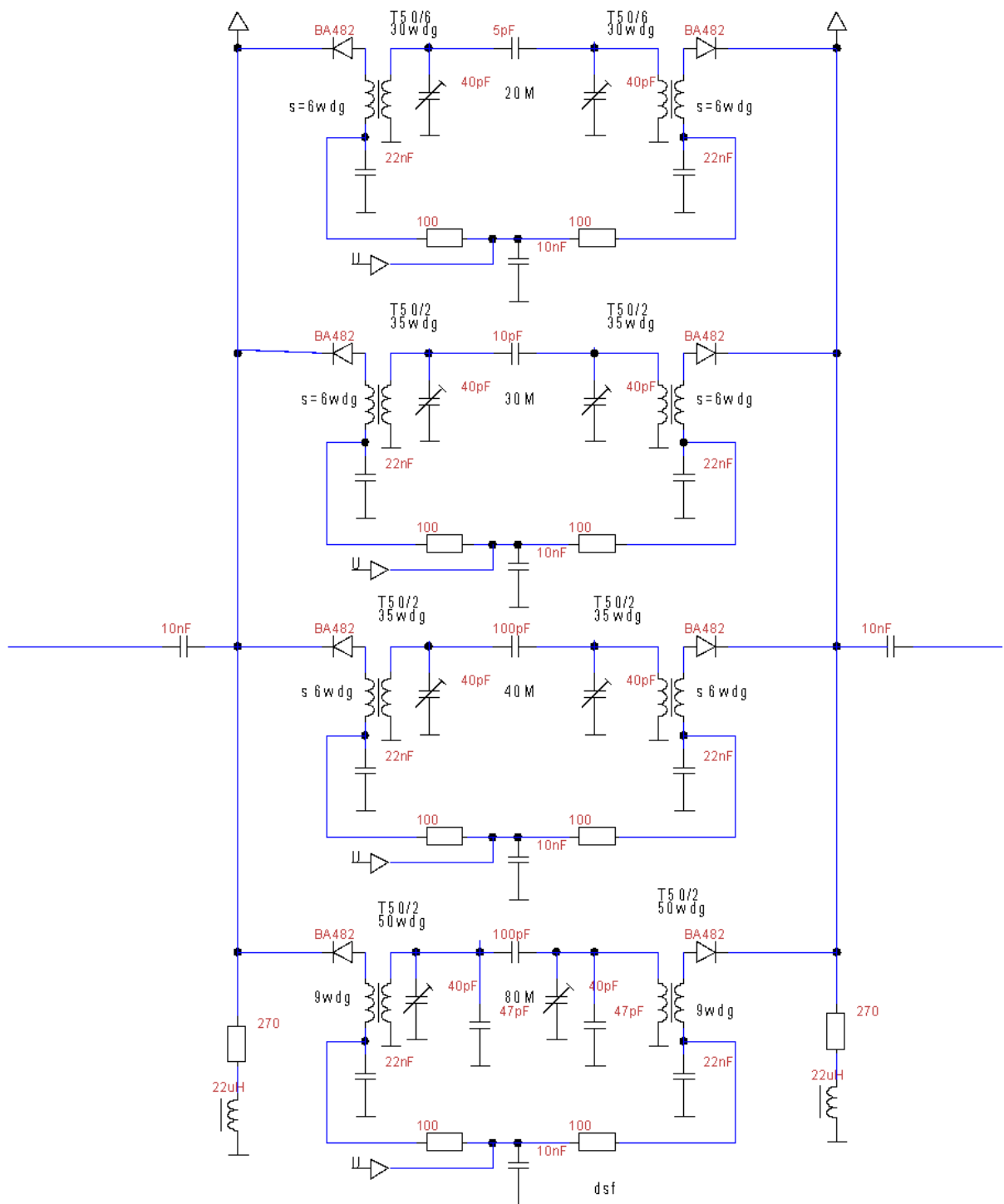

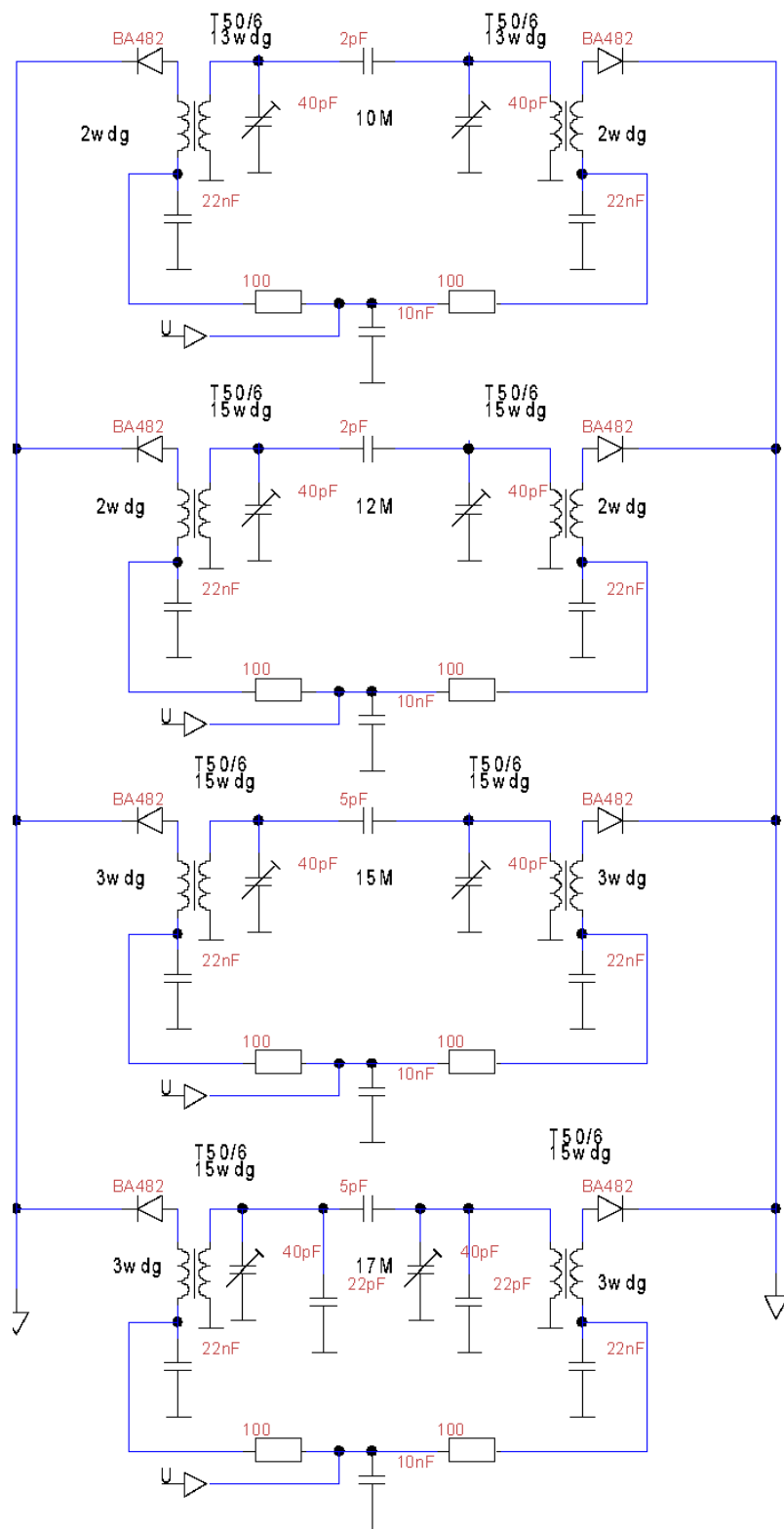


dsf

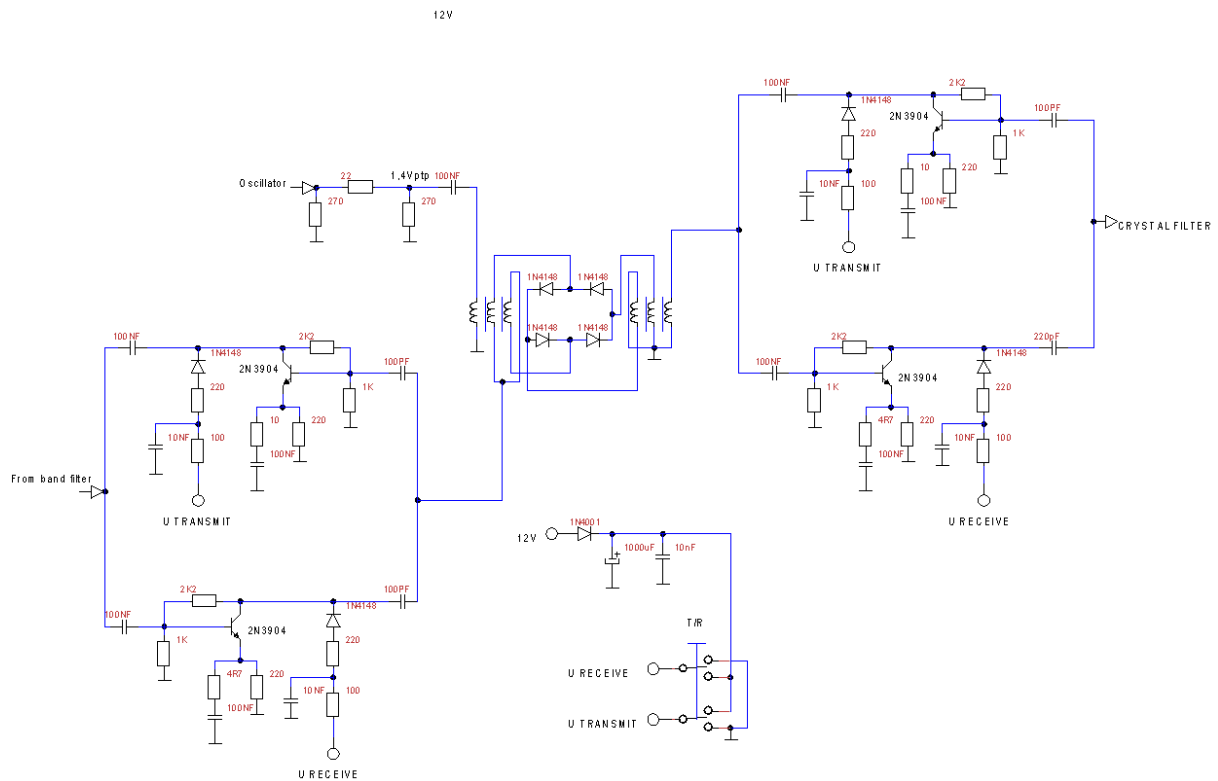


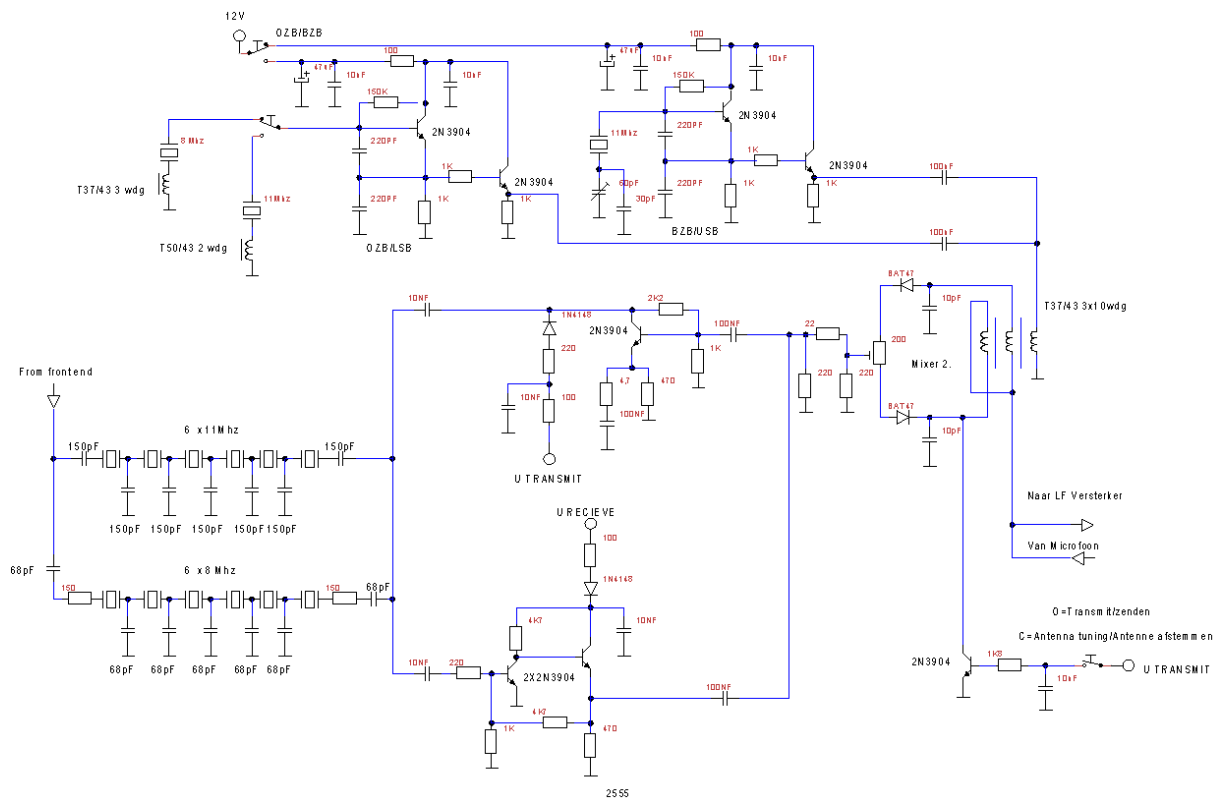Exact copies for the HF amplifier, mixer and IF amplifier of the Bitx schematic.





The amplifiers are exact copies of the Bitx schematic. However because the transceiver is all-band there is also a USB side-band oscillator. the intermediate frequency is 11 Mhz, however this did not work out for 15M. For 15M the LSB sideband oscillator is set on 8Mhz and the signal goes through the 8Mhz crystal filter. As I found out, the two crystal filters can be connected parallel without switches.

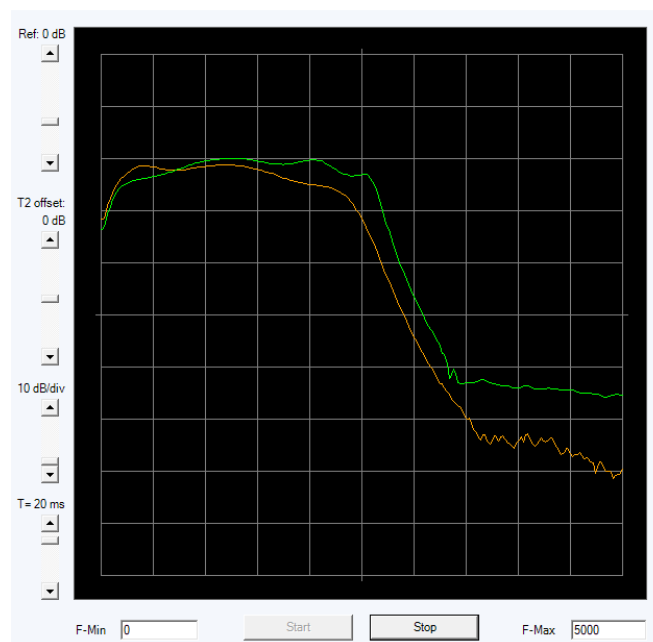

Bandpass 11Mhz. USB groen/ LSB oranje.

Nothing special about the audio sections. I did however needed more microphone amplification than the Bitx schematic suggested.

Also there is a very simple two LED VU meter. When I speak into the microphone at the right distance the green LED lights up. But when I start to speak too loud or too close to the microphone (and clip the signal), the red LED lights up to warn me. In my opinion a very necessary feature.



The microphone was salvaged from a 1980s cassette player...

