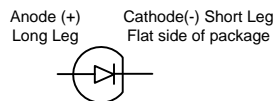


Date	Revision/Addition/ Note	By:
Sep 19 2016	Initial Drawing. A friend of mine who flies drone quad copters wanted to add Red/Green flashing strobes. My design criteria from him, pull every gram weight I could out of it. Must run on 3.7v drone battery. Reduced to 1 chip, 2 LEDS, 1 resistor. Used twisted pair 30ga wire wrap wire soldered right to chip to save weight. Used a JST connector to drone battery	GSC
Sep 19 2016	Software RGstrobe.hex	GSC
Sep 19 2016	12F629 and 12F675 are pin for pin identical. 12F675 has the addition of 4 A/D channels. Used 12F629 for this design.	GSC
Sep 19 2016	Played with the strobe effect and settled on 5 flashes, .05 sec long, with a .05 second pause between flashes. Then pause one second and flash the other Led the same time lengths.	GSC



Drawn By: Gerald Crenshaw WD4BIS	Date: Sep 19 2016	From the bench of: Amateur Radio Station WD4BIS	Page of 1
Designed By: Gerald Crenshaw WD4BIS	Date: Sep 19 2016		Scale: None
Checked By: Janet Crenshaw WB9ZPH	Date: Sep 19 2016	Red Green Strobe	